



**SIMATS SCHOOL OF ENGINEERING**  
**SAVEETHA INSTITUTE OF MEDICAL AND TECHNICAL SCIENCES**  
**CHENNAI-602105**



## **Lab Manual**

### **EEA01 – BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**





## **LIST OF EXPERIMENTS**

1. Verification of Ohm's law & Kirchhoff's law.
2. Verification of current and voltage division rules.
3. Verification of star-delta transformation using resistance reduction technique.
4. Verification of Thevenin's and Norton's Theorems.
5. Verification of Superposition and Maximum power transfer Theorems.
6. Load test on Single Phase Transformer.
7. **O.C.** and **S.C.** test on a single phase transformer.
8. Calculation of Secondary turns and Current in a transformer.
9. Load test on Single phase Induction Motor.
10. Output characteristics of LVDT and calibrate the measuring instruments.
11. Power measurement using two wattmeter methods.
12. Calculate the energy consumption using the Energy meter.
13. Load test on DC shunt Motor.
14. Staircase Wiring & Fluorescent tube wiring
15. Find Stability of a System Using Routh Hurwitz Criterion.
16. Investigating the Performance of Three-Phase Induction Motor Drive Systems in Electric Vehicle Applications.
17. Write SCILAB program to generate the following signals:
  - (a) Unit step signal, (b) Unit Impulse signal , (c) Unit ramp signal,
  - (d) Sinusoidal signal, (e) Exponential signal
18. Write a SCILAB program to obtain the following:
  - (a) DIT-FFT Algorithm (b) DIF-FFT Algorithm
19. Design a filter using the Transformation Method.
  - (a) Bilinear Transformation, (b) Impulse Invariant Transformation
20. Write the SCILAB program to design the following Butterworth filters
  - (a)Low pass filter, (b)High pass filter, (c)Band pass filter
  - (d)Band reject filter.



<b>Expt. No.1</b>	<b>Verification of Ohm's law &amp; Kirchhoff's law</b>
-------------------	--

### 1. (a) Verification of Ohm's law


#### AIM:

To verify Ohm's law for a given resistive network.

#### APPARATUS REQUIRED:

S.No.	Apparatus Name	Range	Quantity
1	RPS	(0-30)V	1
2	Ammeter	(0-200)mA	1
3	Voltmeter	(0-30)V	1
4	Resistor	1KΩ	1
5	Rheostat	300Ω/2A	1
6	Bread board & Connecting wires	--	Required

#### CIRCUIT DIAGRAM:

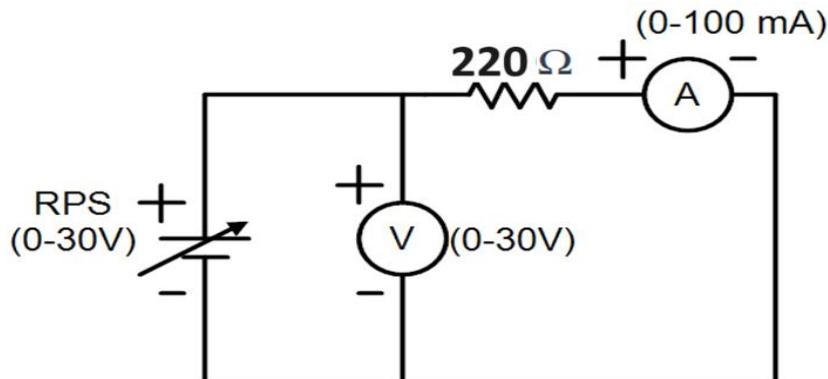

#### PROCEDURE:

1. Make the connections as per circuit diagram.
2. Switch ON the power supply to RPS and apply a voltage (say 10V) and take the reading of voltmeter and ammeter.
3. Adjust the rheostat in steps and take down the readings of ammeter and voltmeter.
4. Plot a graph with V along x-axis and I along y-axis.
5. The graph will be a straight line which verifies Ohm's law.
6. Determine the slope of the V-I graph. The reciprocal of the slope gives resistance of the wire.

## OBSERVATIONS:

S.No.	Voltage (V)	Current (mA)	Experimental Value $R = V/I \text{ in } \Omega$	Theoretical Value $R = V/I \text{ in } \Omega$
1.	1	5	200	
2.	2	10	200	220
				220
4.	4	20	200	220
5.	5	24	208.3	220
6.	6	28	214.28	220
7.	7	32	218.75	220

## THEORETICAL CALCULATIONS

1.  $V=IR$

$$I = \frac{V}{R} = \frac{1}{220} = 4.5454mA$$

$$R = \frac{V}{I} = \frac{1}{4.5454 \times 10^{-3}} = 220\Omega$$

2.  $I = \frac{V}{R} = \frac{2}{220} = 9.0909mA$

$$R = \frac{V}{I} = \frac{2}{9.0909 \times 10^{-3}} = 220\Omega$$

3.  $I = \frac{V}{R} = \frac{3}{220} = 13.6363mA$

$$R = \frac{V}{I} = \frac{3}{13.6363 \times 10^{-3}} = 220\Omega$$

4.  $I = \frac{V}{R} = \frac{4}{220} = 18.1818mA$

$$R = \frac{V}{I} = \frac{4}{18.1818 \times 10^{-3}} = 220\Omega$$

5.  $I = \frac{V}{R} = \frac{5}{220} = 22.7272mA$

$$R = \frac{V}{I} = \frac{5}{22.7272 \times 10^{-3}} = 220\Omega$$



6.  $I = \frac{V}{R} = \frac{6}{220} = 27.2727mA$

$$R = \frac{V}{I} = \frac{6}{27.2727 \times 10^{-3}} = 220\Omega$$

7.  $I = \frac{V}{R} = \frac{7}{220} = 31.8181mA$

$$R = \frac{V}{I} = \frac{7}{31.8181 \times 10^{-3}} = 220\Omega$$

### MODEL GRAPH:

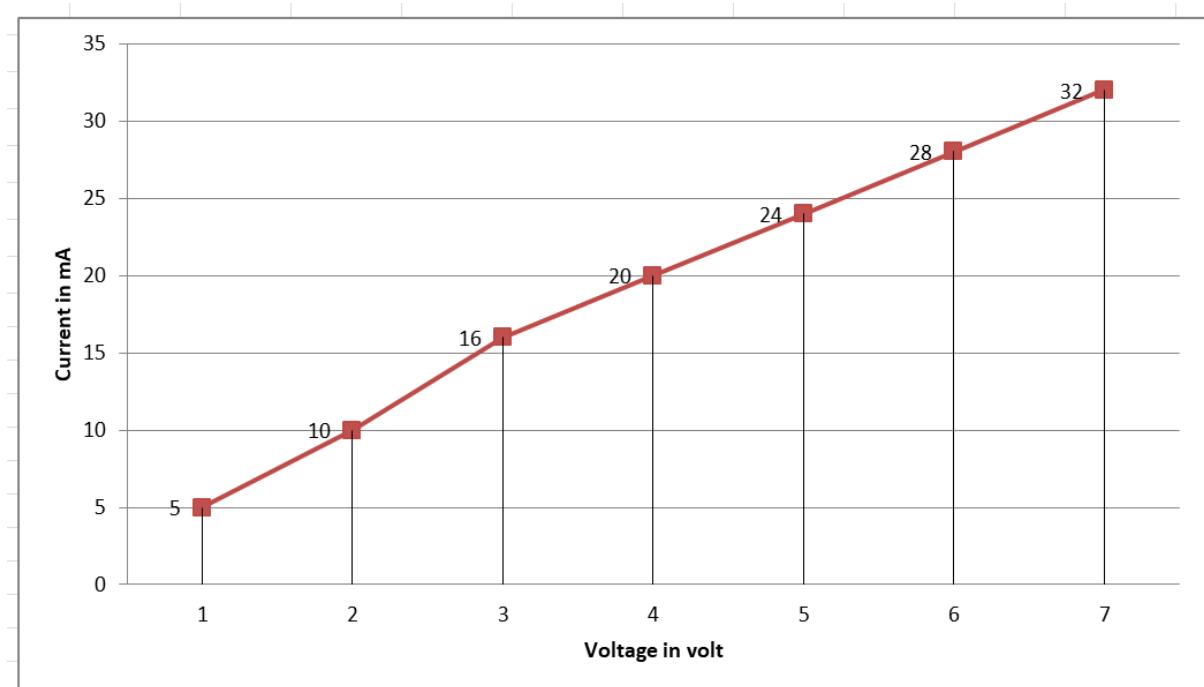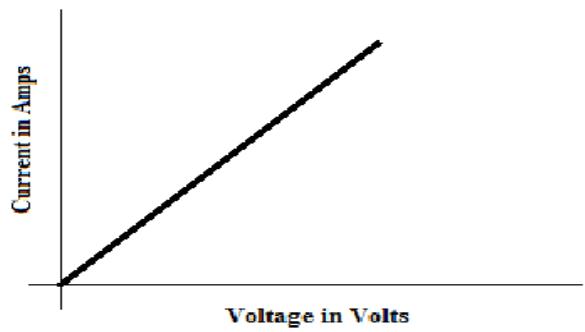

Marks Obtained:

<b>Theoretical Calculations</b>	<b>20</b>	
<b>Observation</b>	<b>20</b>	
<b>Execution of practice examples</b>	<b>30</b>	
<b>Viva</b>	<b>10</b>	
<b>Record</b>	<b>20</b>	
<b>Total Score</b>	<b>100</b>	
<b>Date of experiment</b>		
<b>Date of record submission</b>		<b>Faculty signature</b>

### **RESULT:**

Thus the Ohm's law is verified for the given circuit.

**AIM:**


1. To verify Kirchhoff's voltage law.
2. To verify the Kirchhoff's current law.

**APPARATUS REQUIRED:**

S.No	Name of The Equipment	Type	Range	Qty
1.	RPS	-	(0-15) V	1
2.	Bread board	-	-	1
3.	Ammeter	MC MC	(0-10) mA (0-5) mA	1 2
4.	Voltmeter	MC MC	(0-10)V (0-15) V	1 1
5.	Resistor	-	470Ω , 330Ω, 4kΩ, 4.7kΩ	Each 1
6.	Connecting wires	-	-	As required

**THEORY:****KIRCHHOFF'S VOLTAGE LAW (KVL):**

In any network the algebraic sum of the voltage drops across the circuit elements of any closed path is equal to the algebraic sum of the emf's in the path.

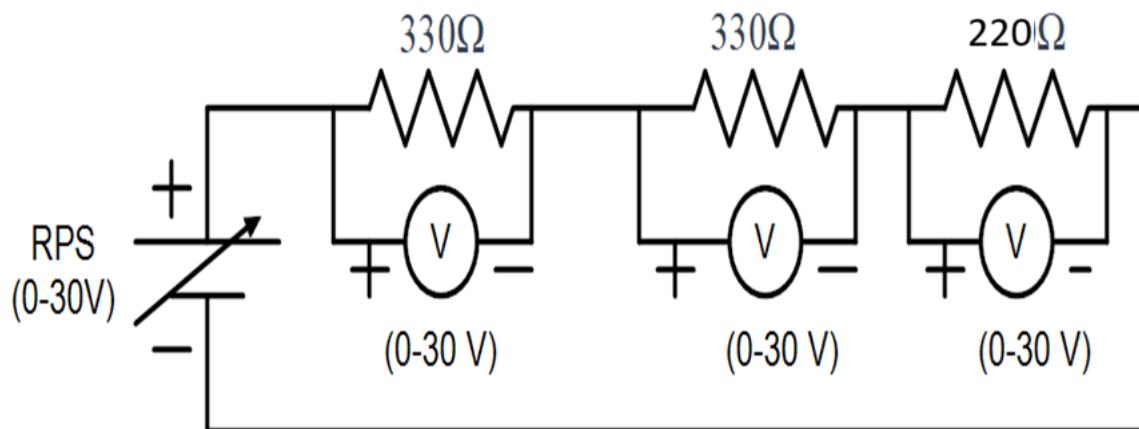**CIRCUIT DIAGRAM FOR KVL:**

### **KIRCHHOFF'S CURRENT LAW (KCL):**

Kirchhoff's Current law states that the algebraic sum of current entering any node is zero. In other words the sum of current going into a node must be equal to current going out from the node.

### **PRECAUTIONS:**

1. Keep RPS at maximum when switching ON and OFF the power supply.
2. Connections should properly check before switch ON the supply.

### **PROCEDURE:**

1. Connections are given as per the circuit diagram.
2. Apply d.c voltage to the circuit from the given RPS.
3. Tabulate the Voltmeters and Ammeters readings for the corresponding experiment.
4. Increase the voltage step by step to get different readings till the voltage reached up to 15V.
5. Repeat step 3 for different values.
6. Switch OFF the power supply after bringing RPS to the minimum voltage position.

Tabulation for KVL:

Parameter	Experimental Value				Theoretical Value			
	Voltage Across R <sub>1</sub>	Voltage Across R <sub>2</sub>	Voltage Across R <sub>3</sub>	Loop Current(mA)	Voltage Across R <sub>1</sub>	Voltage Across R <sub>2</sub>	Voltage Across R <sub>3</sub>	Loop Current(mA)
20V	7.2	7.3	4.5	21	7.5V	7.5V	5V	22.73

Theoretical Calculation:

$$V = 20V$$

$$R = R_1 + R_2 + R_3$$

$$R = 330 + 330 + 220 = 880\Omega$$

$$I = \frac{V}{R} = \frac{20}{880} = 0.02273A = 22.73mA$$

$$V_1 = IR_1 = 0.02273 \times 330 = 7.5V$$


$$V_2 = IR_2 = 0.02273 \times 330 = 7.5V$$

$$V_3 = IR_3 = 0.02273 \times 220 = 5V$$

$$V = V_1 + V_2 + V_3$$

$$V = 7.5 + 7.5 + 5 = 20V$$
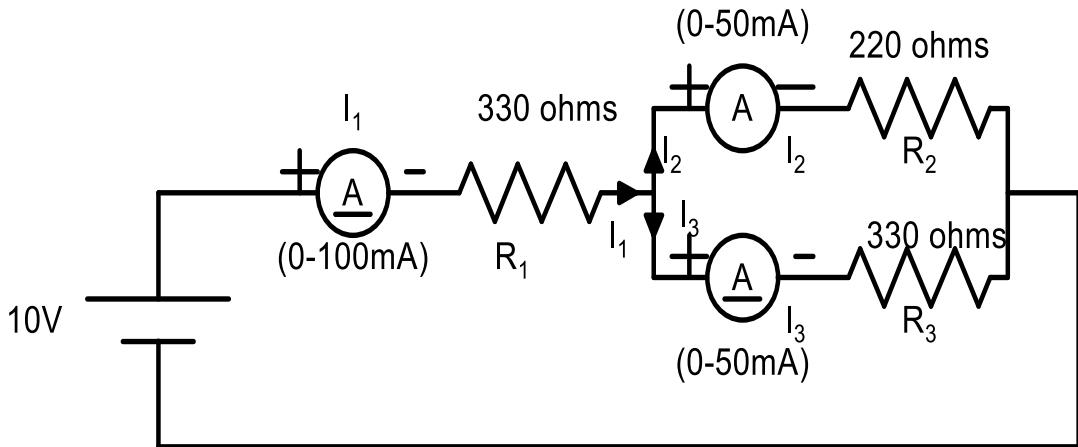
### 1. (b) Verification of Kirchhoff's Current Law



Tabulation for KCL:

Parameter	Experimental Value				Theoretical Value			
Supply voltage	Current I <sub>1</sub> (mA)	Current I <sub>2</sub> (mA)	Current I <sub>3</sub> (mA)	I <sub>2</sub> + I <sub>3</sub> (mA)	Current I <sub>1</sub> (mA)	Current I <sub>2</sub> (mA)	Current I <sub>3</sub> (mA)	I <sub>2</sub> + I <sub>3</sub>
10V	19.5	11.5	8	19.5	21.64	12.98	8.6575	21.64

Theoretical Calculation:

To Find R<sub>eq</sub>:

$$R_{eq} = R_1 + R_2 \parallel R_3$$

$$R_{eq} = 330 + 220 \parallel 330$$

$$R_{eq} = 330 + \left( \frac{220 \times 330}{220 + 330} \right) = 462\Omega$$

$$V = 10V$$

$$I = \frac{V}{R} = \frac{10}{462} = 0.02164A = 21.64mA$$

$$V_1 = I_1 R_1 = 0.02164 \times 330 = 7.14V$$

$$V = V_1 + V_2$$

$$10 = 7.14 + V_2$$

$$V_2 = 2.857V$$

$$I_2 = \frac{V_2}{R_2} = \frac{2.857}{220} = 0.01298 = 12.98mA$$

$$I_3 = \frac{V_3}{R_3} = \frac{2.857}{330} = 8.6575mA$$

sum of incoming current = sum of outgoing current

$$I_1 = I_2 + I_3$$

$$I_1 = 12.98 + 8.657 = 21.64mA$$

Marks Obtained:

<b>Theoretical Calculations</b>	<b>20</b>	
<b>Observation</b>	<b>20</b>	
<b>Execution of practice examples</b>	<b>30</b>	
<b>Viva</b>	<b>10</b>	
<b>Record</b>	<b>20</b>	
<b>Total Score</b>	<b>100</b>	
<b>Date of experiment</b>		
<b>Date of record submission</b>		<b>Faculty signature</b>

### **RESULT:**



Thus the Kirchhoff's voltage and current law is verified for the given circuit.

**Expt. No. 02****Verification of current and voltage division rules****AIM:**

To calculate the individual branch currents and total current drawn from the power supply using current and voltage division rules.

**APPARATUS REQUIRED:**

S.No.	Apparatus Name	Range	Quantity
1	DC Regulated Power Supply	(0-30)V	1
2	Ammeter	(0-200)mA	4
3	Resistor	1k $\Omega$ , 220 $\Omega$	Each two
4	Bread board & Connecting wires	--	Required

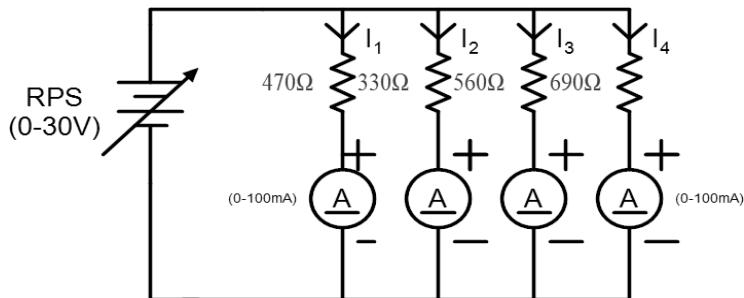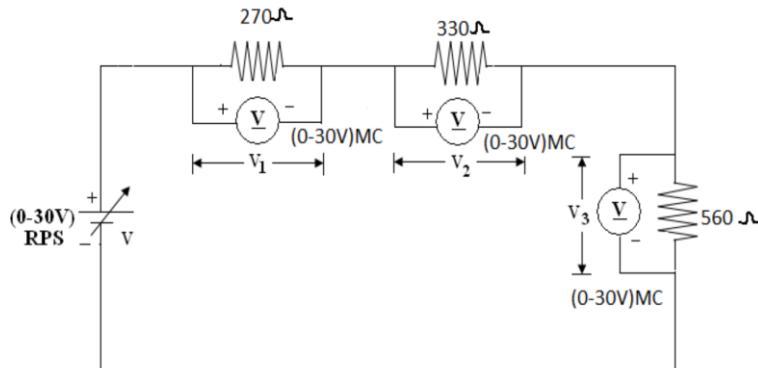**CIRCUIT DIAGRAM:****CURRENT DIVISION CIRCUIT DIAGRAM:****Voltage Division Circuit Diagram:****PROCEDURE:**

1. Give the connections as per the circuit diagram.
2. Set a particular value in RPS.
3. Note down the corresponding ammeter reading
4. Repeat the same for different voltages

## OBSERVATIONS:

### CURRENT DIVISION RULE:

S. No.	Voltage (V)	Current (mA)			
		I <sub>1</sub>	I <sub>2</sub>	I <sub>3</sub>	I <sub>4</sub>
1	1	5	10.64	15.15	8.93
2	2	10	21.28	30.3	17.86
3	3	15	31.91	45.45	26.79
4	4	20	42.55	60.61	35.71
5	5	25	53.19	75.76	44.64

### VOLTAGE DIVISION RULE:

S. No.	RPS Voltage (V)	Voltage across Resistors (V)			V <sub>1</sub> +V <sub>2</sub> +V <sub>3</sub> (V)
		V <sub>1</sub>	V <sub>2</sub>	V <sub>3</sub>	
1	5	1.16	1.42	2.41	5
2	10	2.32	2.84	4.83	10
3	15	3.49	4.26	7.24	15
4	20	4.65	5.68	9.66	20
5	25	5.81	7.1	12.07	25

## MODEL CALCULATIONS:

### CURRENT DIVISION RULE:

#### For Voltage (V) = 5V:

Resistor R<sub>1</sub> = 470 Ω:

$$I_1 = V / R_1 = 5V / 470\Omega = 10.64 \text{ mA}$$

Resistor R<sub>2</sub> = 330 Ω:

$$I_2 = V / R_2 = 5V / 330\Omega = 15.15 \text{ mA}$$

Resistor R<sub>3</sub> = 560 Ω:

$$I_3 = V / R_3 = 5V / 560\Omega = 8.93 \text{ mA}$$

Resistor R<sub>4</sub> = 690 Ω:

$$I_4 = V / R_4 = 5V / 690\Omega = 7.25 \text{ mA}$$

#### For Voltage (V) = 10V:

Resistor R<sub>1</sub> = 470 Ω:

$$I_1 = V / R_1 = 10V / 470\Omega = 21.28 \text{ mA}$$

Resistor R<sub>2</sub> = 330 Ω:

$$I_2 = V / R_2 = 10V / 330\Omega = 30.30 \text{ mA}$$

Resistor R<sub>3</sub> = 560 Ω:

$$I_3 = V / R_3 = 10V / 560\Omega = 17.86 \text{ mA}$$

Resistor R4 = 690 Ω:  
 $I_4 = V / R_4 = 10V / 690\Omega = 14.49 \text{ mA}$

### For Voltage (V) = 15V:

Resistor R1 = 470 Ω:  
 $I_1 = V / R_1 = 15V / 470\Omega = 31.91 \text{ mA}$   
Resistor R2 = 330 Ω:  
 $I_2 = V / R_2 = 15V / 330\Omega = 45.45 \text{ mA}$   
Resistor R3 = 560 Ω:  
 $I_3 = V / R_3 = 15V / 560\Omega = 26.79 \text{ mA}$   
Resistor R4 = 690 Ω:  
 $I_4 = V / R_4 = 15V / 690\Omega = 21.74 \text{ mA}$

### For Voltage (V) = 20V:

Resistor R1 = 470 Ω:  
 $I_1 = V / R_1 = 20V / 470\Omega = 42.55 \text{ mA}$   
Resistor R2 = 330 Ω:  
 $I_2 = V / R_2 = 20V / 330\Omega = 60.61 \text{ mA}$   
Resistor R3 = 560 Ω:  
 $I_3 = V / R_3 = 20V / 560\Omega = 35.71 \text{ mA}$   
Resistor R4 = 690 Ω:  
 $I_4 = V / R_4 = 20V / 690\Omega = 28.99 \text{ mA}$

### For Voltage (V) = 25V:

Resistor R1 = 470 Ω:  
 $I_1 = V / R_1 = 25V / 470\Omega = 53.19 \text{ mA}$   
Resistor R2 = 330 Ω:  
 $I_2 = V / R_2 = 25V / 330\Omega = 75.76 \text{ mA}$   
Resistor R3 = 560 Ω:  
 $I_3 = V / R_3 = 25V / 560\Omega = 44.64 \text{ mA}$   
Resistor R4 = 690 Ω:  
 $I_4 = V / R_4 = 25V / 690\Omega = 36.23 \text{ mA}$

## VOLTAGE DIVISION RULE:

### For RPS Voltage (V) = 5V:

Voltage across Resistor R1 (270 Ω):  
 $V_1 = 5 * (270 / 1160) = 1.16 \text{ V}$   
Voltage across Resistor R2 (330 Ω):  
 $V_2 = 5 * (330 / 1160) = 1.42 \text{ V}$   
Voltage across Resistor R3 (560 Ω):  
 $V_3 = 5 * (560 / 1160) = 2.41 \text{ V}$

Check:  $V_1 + V_2 + V_3 = 1.16 + 1.42 + 2.41 = 5.00 \text{ V}$

### For RPS Voltage (V) = 10V:

Voltage across Resistor R1 (270 Ω):

$$V1 = 10 * (270 / 1160) = 2.33 \text{ V}$$

Voltage across Resistor R2 ( $330 \Omega$ ):

$$V2 = 10 * (330 / 1160) = 2.84 \text{ V}$$

Voltage across Resistor R3 ( $560 \Omega$ ):

$$V3 = 10 * (560 / 1160) = 4.83 \text{ V}$$

Check:  $V1 + V2 + V3 = 2.33 + 2.84 + 4.83 = 10.00 \text{ V}$

### For RPS Voltage (V) = 15V:

Voltage across Resistor R1 ( $270 \Omega$ ):

$$V1 = 15 * (270 / 1160) = 3.49 \text{ V}$$

Voltage across Resistor R2 ( $330 \Omega$ ):

$$V2 = 15 * (330 / 1160) = 4.27 \text{ V}$$

Voltage across Resistor R3 ( $560 \Omega$ ):

$$V3 = 15 * (560 / 1160) = 7.24 \text{ V}$$

Check:  $V1 + V2 + V3 = 3.49 + 4.27 + 7.24 = 15.00 \text{ V}$

### For RPS Voltage (V) = 20V:

Voltage across Resistor R1 ( $270 \Omega$ ):

$$V1 = 20 * (270 / 1160) = 4.66 \text{ V}$$

Voltage across Resistor R2 ( $330 \Omega$ ):

$$V2 = 20 * (330 / 1160) = 5.69 \text{ V}$$

Voltage across Resistor R3 ( $560 \Omega$ ):

$$V3 = 20 * (560 / 1160) = 9.66 \text{ V}$$

Check:  $V1 + V2 + V3 = 4.66 + 5.69 + 9.66 = 20.00 \text{ V}$

### For RPS Voltage (V) = 25V:

Voltage across Resistor R1 ( $270 \Omega$ ):

$$V1 = 25 * (270 / 1160) = 5.82 \text{ V}$$

Voltage across Resistor R2 ( $330 \Omega$ ):

$$V2 = 25 * (330 / 1160) = 7.11 \text{ V}$$

Voltage across Resistor R3 ( $560 \Omega$ ):

$$V3 = 25 * (560 / 1160) = 12.07 \text{ V}$$

Check:  $V1 + V2 + V3 = 5.82 + 7.11 + 12.07 = 25.00 \text{ V}$

## RESULT:

Thus, the individual branch currents and total current drawn from the power supply are calculated using current and voltage division rules.

**Expt. No. 03**

**Verification of star delta transformation**


**AIM:**

To calculate the equivalent circuit resistance using star delta transformation technique.

**APPARATUS REQUIRED:**

S.No.	Apparatus Name	Range	Quantity
1	Resistor		
2	Bread board & Connecting wires	--	Required

**CIRCUIT DIAGRAM:**


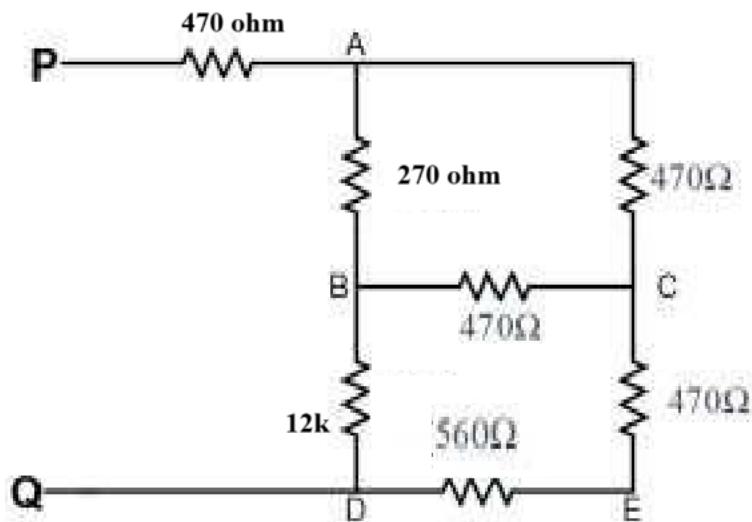


**PROCEDURE:**

1. Give the connections as per the circuit diagram.
2. Determine the equivalent resistance of the circuit between P and Q using star – delta transformation technique
3. Verify the same by connecting multimeter across PQ

Theoretical Calculation

Circuit Diagram:

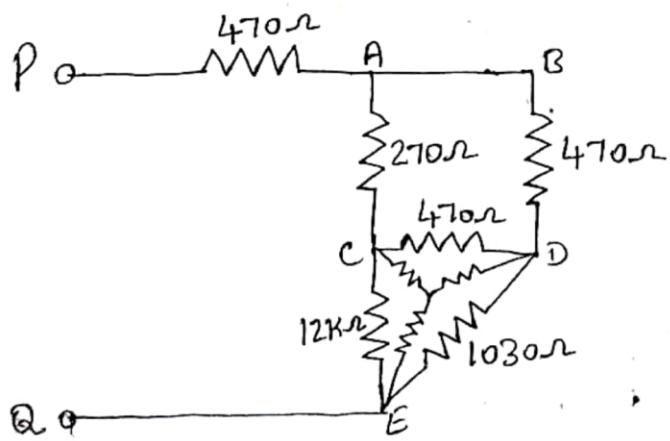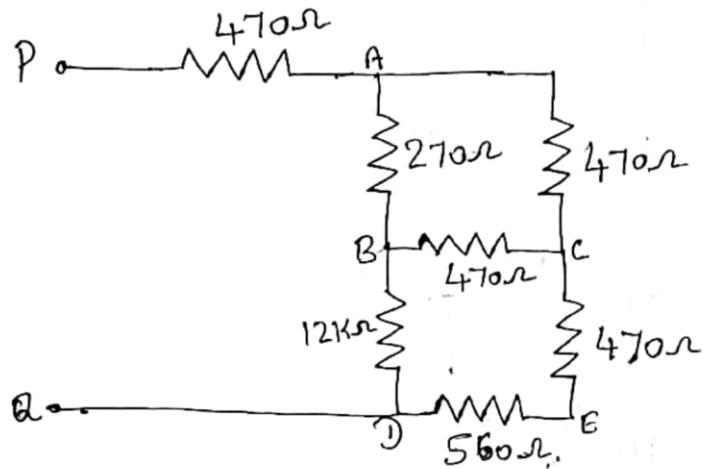

$$R_C = \frac{R_{CB} R_{CD}}{R_{CE} + R_{ED} + R_{CD}}$$

$$R_C = \frac{12 \times 10^3 \times 470}{470 + 1030 + (12 \times 10^3)}$$



$R_C = 417.77 \Omega$


$$R_E = \frac{R_{CE} \cdot R_{ED}}{R_{CE} + R_{ED} + R_{CD}} = \frac{12 \times 10^3 \times 1030}{(12 \times 10^3) + 1030 + 470}$$

$$R_E = 915.55 \Omega$$

$$R_D = \frac{R_{CD} R_{DE}}{R_{CE} + R_{ED} + R_{CD}} = \frac{470 \times 1030}{(12 \times 10^3) + 1030 + 470}$$

$$R_D = 35.859 \Omega$$

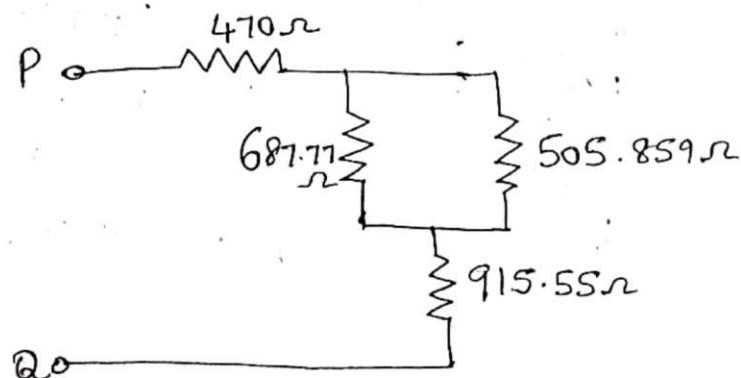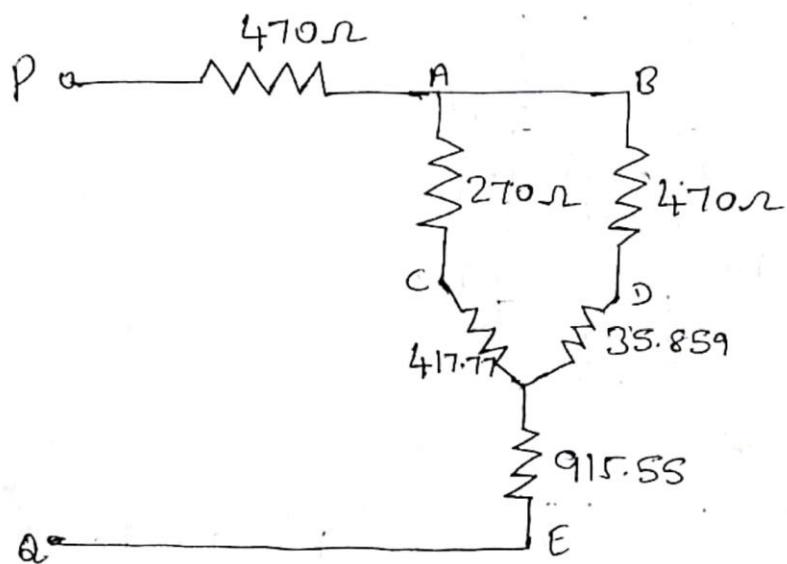

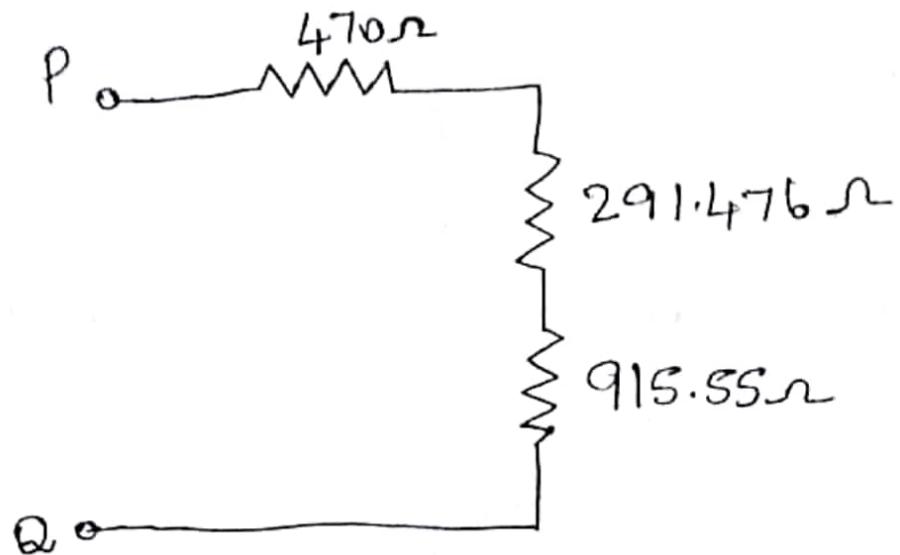

$$R_{PQ} = 1.677 \text{ k}\Omega$$

$R_{PQ} = 1.7 \text{ k}\Omega$

#### OBSERVATIONS:

S.No.	Theoretical value ( $R_{PQ}$ ) in ohm	Measured value ( $R_{PQ}$ ) in ohm
1		

#### RESULT:

Thus the equivalent circuit resistance is obtained using star delta transformation technique.

# BASIC ELECTRICAL AND ELECTRONICS ENGINEERING LAB

<b>Expt. No. 04</b>	<b>Verification of Thevenin's and Norton's Theorems</b>
---------------------	---


## **AIM:**

To verify the equivalent circuit parameters of Thevenin's and Norton's Theorems theoretically and practically.

## **APPARATUS REQUIRED:**

S.No.	Apparatus Name	Range	Quantity
1	DC Regulated Power Supply	(0-30)V	1
2	Voltmeter	(0-30)V	1
3	Ammeter	(0-200)mA	1
4	Resistor	$330\Omega, 220\Omega, 470 \Omega, 560 \Omega, 100 \Omega$	As required
5	Multimeter	-	1
6	Bread board & Connecting wires	--	As Required

## **CIRCUIT DIAGRAM:**

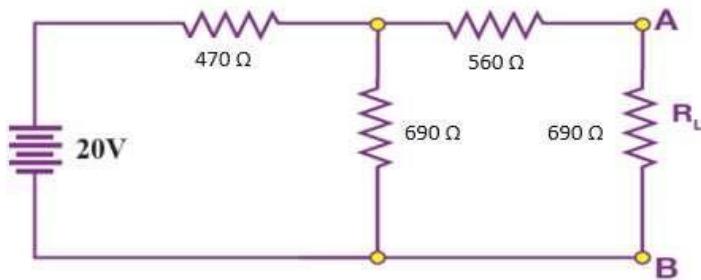


## **PROCEDURE FOR THEVENIN'S THEOREM:**

1. Give the connections as per the circuit diagram.
2. Measure  $R_{th}$  using a multimeter by killing sources (O.C the current source and S.C the voltage source) and open circuit  $R_L$ .
3. Measure  $V_{th}$  across A & B (open circuit  $R_L$ )
4. Measure load current  $I_L$  through  $R_L$ .

$$I_L = \frac{V_{th}}{R_{th} + R_L}$$

5. Draw the Thevenin's Equivalent Circuit.
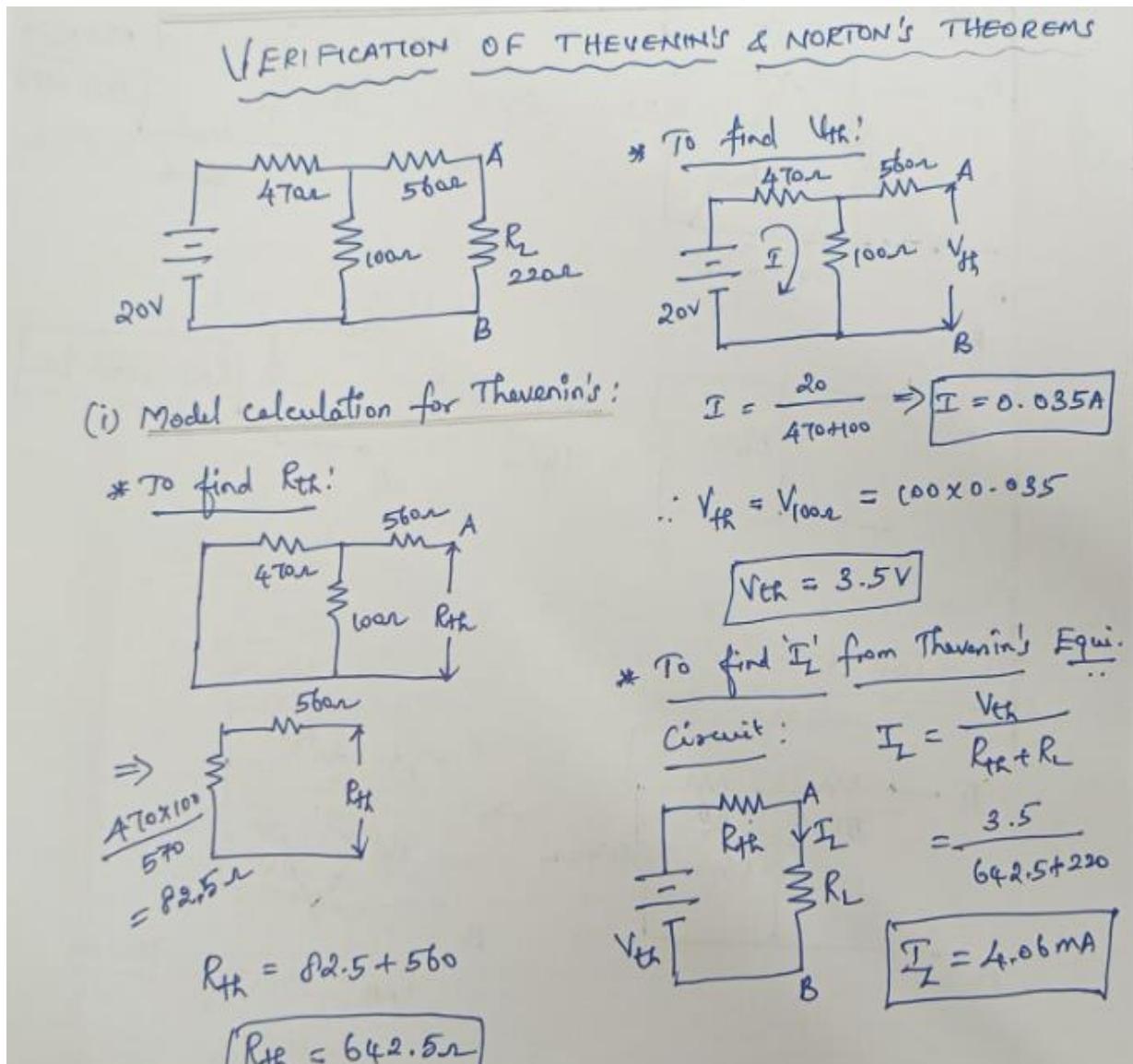
## MODEL CALCULATION: THEVENIN'S THEOREM:



## OBSERVATIONS:

S.No.	Supply Voltage (V)	Theoretical values			Measured values		
		$R_{th}(\Omega)$	$V_{th}(V)$	$I_L(mA)$	$R_{th}(\Omega)$	$V_{th}(V)$	$I_L(mA)$
1	20	642.5	3.5	4.06	640	3.5	4.0

## PROCEDURE FOR NORTON'S THEOREM:

1. Give the connections as per the circuit diagram.
2. Measure  $R_{th}$  using a multimeter by killing sources (O.C the current source and S.C the voltage source) and open circuit  $R_L$ .
3. Measure  $I_N$  through A & B (Short circuit  $R_L$ )
4. Measure load current  $I_L$  through  $R_L$ .
5. Draw the Norton's Equivalent Circuit.

## MODEL CALCULATION: NORTON'S THEOREM:

(ii) Model calculation for Norton's :

\*  $R_{th} = 642.5\Omega$  (Same as Thvenin's)

\* To find  $I_{sc}$  or  $I_L$ :

$$I_T = \frac{V}{R_{eq}} = \frac{20}{554.85} = 0.036A$$

$$R_{eq} = 47 + (56 \parallel 100) = 554.85\Omega$$

$$I_{sc} = \frac{I_T}{R_{th}} \times R_{th} = \frac{0.036}{642.5} \times 642.5 = 5.455mA$$

$$I_L = \frac{(5.455 \times 10^{-3}) \times 642.5}{(642.5 + 20)} = 4.063mA$$

Norton's Equivalent circuit

By current division rule:

$$I_{sc} = I_{56\Omega} = \frac{I_T}{R_{th}} \times R_{th}$$

$$I_{sc} = \frac{0.036}{(100 + 56)} \times 100 = 5.455mA$$

## OBSERVATIONS:

S.No.	Supply Voltage (V)	Theoretical values			Measured values		
		$R_{th}(\Omega)$	$I_{sc}(mA)$	$I_L(mA)$	$R_{th}(\Omega)$	$I_{sc}(mA)$	$I_L(mA)$
1	20	642.5	5.455	4.063	640	5.5	4.0

## RESULT:

Thus the equivalent circuit parameters are obtained using Thevenin's and Norton's Theorem.

<b>Expt. No. 05</b>	<b>Verification of Maximum Power Transfer theorem and Superposition theorem</b>
---------------------	---

### **5(a). Verification of Maximum Power Transfer**


### Theorem AIM:

To verify Maximum Power Transfer Theorem

### **APPARATUS REQUIRED:**

S.No.	Apparatus Name	Range	Quantity
1	DC Regulated Power Supply	(0-30)V	1
2	Voltmeter	(0-30)V	1
3	Ammeter	(0-200)mA	1
4	Resistor	330Ω, 220Ω	Each two
5	Multimeter	-	1
6	Bread board & Connecting wires	--	Required

#### **CIRCUIT DIAGRAM:**

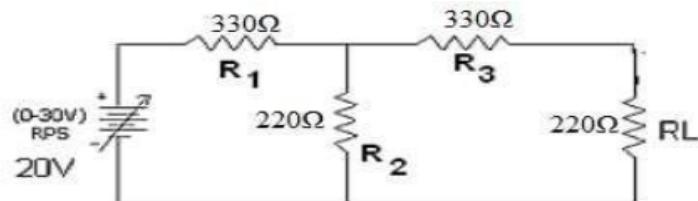


#### **PROCEDURE:**

1. Give the connections as per the circuit diagram.
  2. Measure  $R_{th}$  using a multimeter
  3. Measure  $V_{th}$  across  $220\Omega$  ( $R_2$ )
  4. Measure load current  $I_L$  through  $R_L$
  5. Calculate the maximum power transferred to the load


## OBSERVATIONS:

Manual Calculation:

Maximum Power Transfer

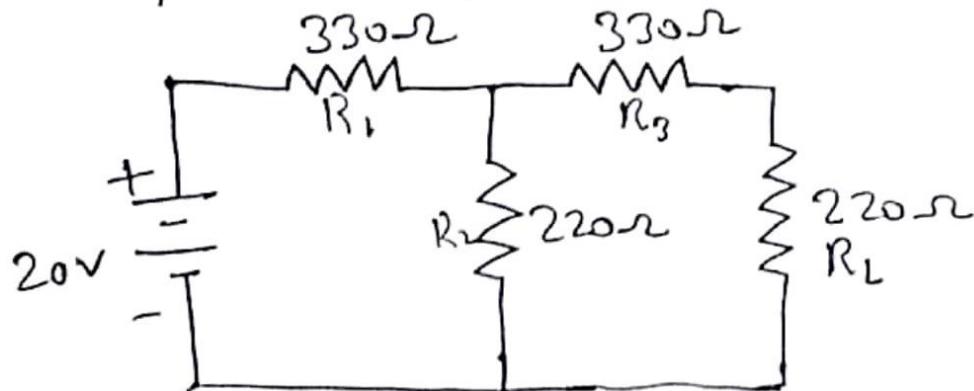


To find  $R_K$

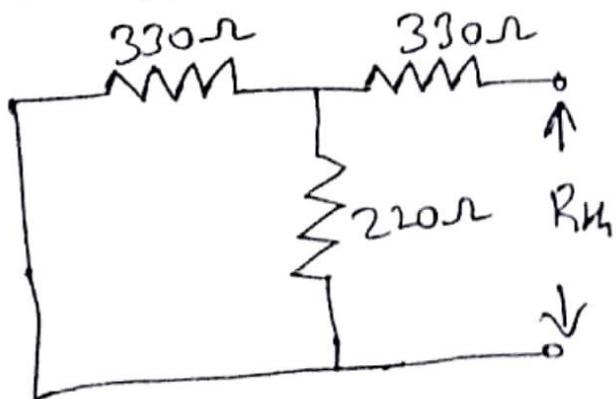

$$R_K = 330 \parallel 220 + 330$$

$$R_K = 462 \Omega$$

To find  $V_{th}$

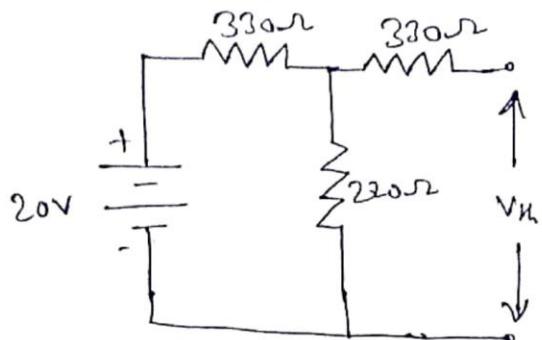

$$V = IR$$


$$I = \frac{V}{R} = \frac{20}{330+220} = 0.03636 \text{ A}$$

$$V_{th} = I R$$


$$= 0.03636 \times 220$$

$V_{th} = 8 \text{ V}$

Thevenin Equivalent circuit

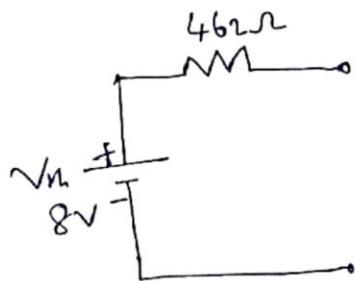

To find load current

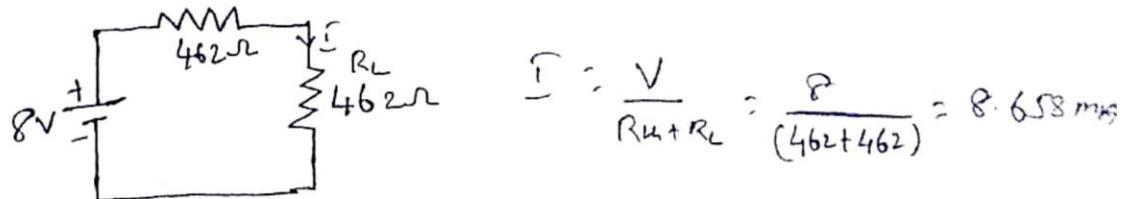

To find maximum power

$$P_{\max} = \frac{V^2}{4R} = \frac{8^2}{4 \times 462} = 0.03463 \text{ W}$$

$$P_{\max} = 34.63 \text{ mW}$$

S.no	V (v)	R ( $\Omega$ )	$I_L$ (mA)	$P_{\max}$ (mw)
------	----------	-------------------	---------------	--------------------

1. 8 150 13.072 25.63

2. 8 300 10.498 33.06

3. 8 450 8.77 34.61


4. 8 462 8.658 34.63  $R_H = R_L$

5. 8 500 8.316 34.57

6. 8 650 7.194 33.63

7. 8 800 6.339 32.146

**MODEL GRAPH:**

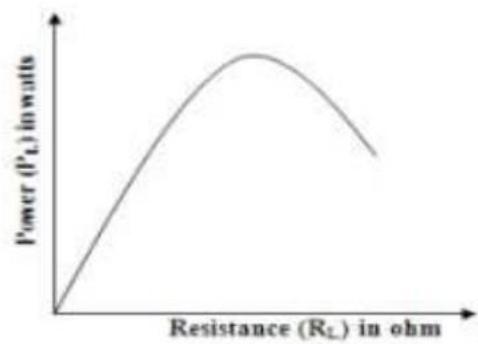

**RESULT:**

Thus the Maximum Power Transfer Theorem is verified.


### 5(b). Verification of Superposition Theorem

**AIM:** To determine the current flow through the load resistor using Superposition Theorem

#### APPARATUS REQUIRED:

S.No.	Apparatus Name	Range	Quantity
1	DC Regulated Power Supply	(0-30)V	2
2	Voltmeter	(0-30)V	1
3	Ammeter	(0-200)mA	1
4	Resistor	1kΩ, 220Ω, 330 Ω	Each one
5	Multimeter	-	1
6	Bread board & Connecting wires	--	Required

Circuit Diagram:

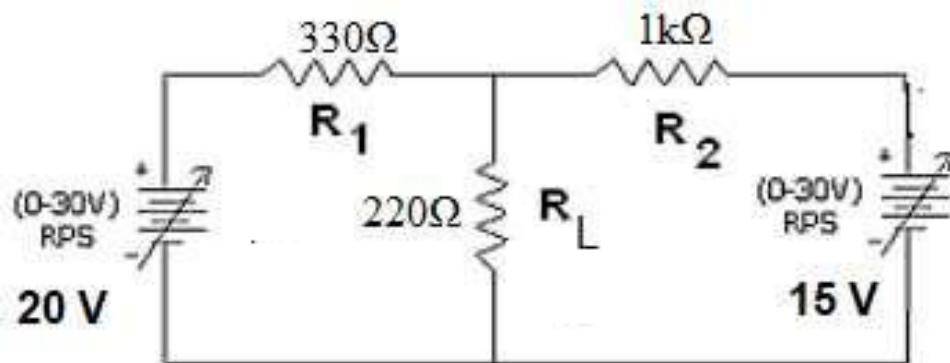


#### PROCEDURE:


1. Give the connections as per the circuit diagram.
2. Measure current flow through  $220\Omega$  by connecting both the supplies.
3. Short circuit 15 V source.
4. Measure current flow through  $220\Omega$  by connecting 20 V supply.
5. Short circuit 20 V source.
6. Measure current flow through  $220\Omega$  by connecting 15 V supply.
7. Verify the net current through  $220\Omega$  resistor.

**CALCULATION:**

Manual Calculation

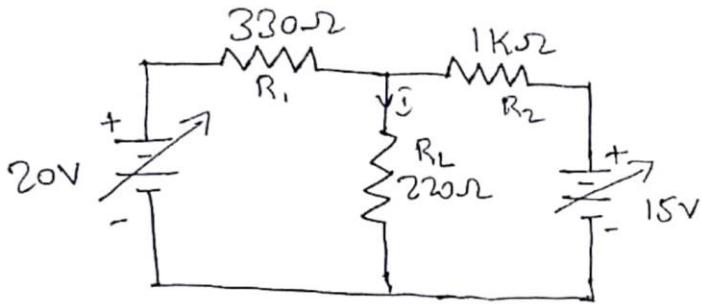

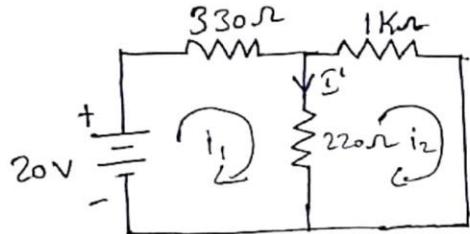[Case(i)] Find Current through  $220\Omega$  by connecting 20V Supply (sc 15V)



$$V = IR$$

$$\begin{bmatrix} 550 & -220 \\ -220 & 1220 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 550 & -220 \\ -220 & 1220 \end{bmatrix} = 671000 - 48400 = 622600$$

$$\Delta_1 = \begin{bmatrix} 20 & -220 \\ 0 & 1220 \end{bmatrix} = 24400$$


$$\Delta_2 = \begin{bmatrix} 550 & 20 \\ -220 & 0 \end{bmatrix} = 4400$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{24400}{622600} = 0.03919 A$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{4400}{622600} = 7.067 \text{ mA}$$

$$I' = 39.19 - 7.067 = 32.123 \text{ mA}$$

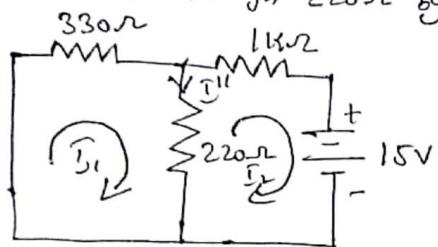(Case iii) Find Current through  $220\Omega$  by connecting 15V supply (S.C 20V)



$$V = IR$$

$$\begin{bmatrix} 550 & -220 \\ -220 & 1220 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -15 \end{bmatrix}$$

$$\Delta = \begin{bmatrix} 550 & -220 \\ -220 & 1220 \end{bmatrix} = 671000 - 48400 = 622600$$

$$\Delta_1 = \begin{bmatrix} 0 & -220 \\ -15 & 1220 \end{bmatrix} = -3300$$

$$\Delta_2 = \begin{bmatrix} 550 & 0 \\ -220 & -15 \end{bmatrix} = -8250$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{-3300}{622600} = -5.3004 \text{ mA}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-8250}{622600} = -13.25 \text{ mA}$$

$$\hat{I}'' = \hat{I}_1 - \hat{I}_2$$

$$= -5.3004 + 13.25$$

$$\hat{I}'' = 7.9496 \text{ mA}$$

By Superposition Theorem

$$\hat{I} = \hat{I}' + \hat{I}''$$

$$\hat{I} = 32.123 + 7.9496$$

$$\hat{I} = 40.0726 \text{ mA}$$

**Find net current**

**OBSERVATIONS:**

S.No.	Measured Current (mA) through $1k\Omega$ when both supplies are connected	Calculated Current (mA) through $1k\Omega$		Measured Current (mA) through $1k\Omega$		Net current (mA)
		V= 20 V	V= 15 V	V= 20 V	V= 15 V	
1.						

**RESULT:**

Thus the current flow through the load resistor is determined using Superposition Theorem.

<b>Expt. No. 6</b>	<b>Load Test on a single phase transformer</b>
--------------------	--

### **AIM:**

To conduct load test on single phase transformer and to find efficiency and percentage regulation.

### **APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-10)A (0-5) A	MI MI	1 1
2	Voltmeter	(0-150)V (0-300) V	MI MI	1 1
3	Wattmeter	(300V, 5A) (150V, 5A)	Upf Upf	1 1
4	Auto Transformer	1ϕ, (0-260)V	-	1
5	Resistive Load	5KW, 230V	-	1
6	Connecting Wires	2.5sq.mm	Copper	Few

### **PRECAUTIONS:**

1. Auto Transformer should be in minimum position.
2. The AC supply is given and removed from the transformer under no load condition.

### **NAME PLATE DETAILS:**

- KVA Rating : .....
- Rated H.V side Voltage : .....
- Rated H.V side Current : .....
- Rated L.V side Voltage : .....
- Rated L.V side Current : .....

### **FUSE RATING CALCULATIONS:**

The required fuse ratings for O.C. are 20 % of rated current on L.V side

$$= \frac{(20/100)}{100} \times \text{Rated current on L.V. Side}$$

$$=$$

The required fuse ratings for S.C. are 120 % of rated current on H.V side


$$= \frac{(120/100)}{100} \times \text{Rated current on H.V. Side}$$

$$=$$

## PROCEDURE:

1. Connections are made as per the circuit diagram.
2. After checking the no load condition, minimum position of auto transformer and DPST switch is closed.
3. Ammeter, Voltmeter and Wattmeter readings on both primary side and secondary side are noted.
4. The load is increased and for each load, Voltmeter, Ammeter and Wattmeter readings on both primary and secondary sides are noted.
5. Again no load condition is obtained and DPST switch is opened.

## CIRCUIT DIAGRAM:

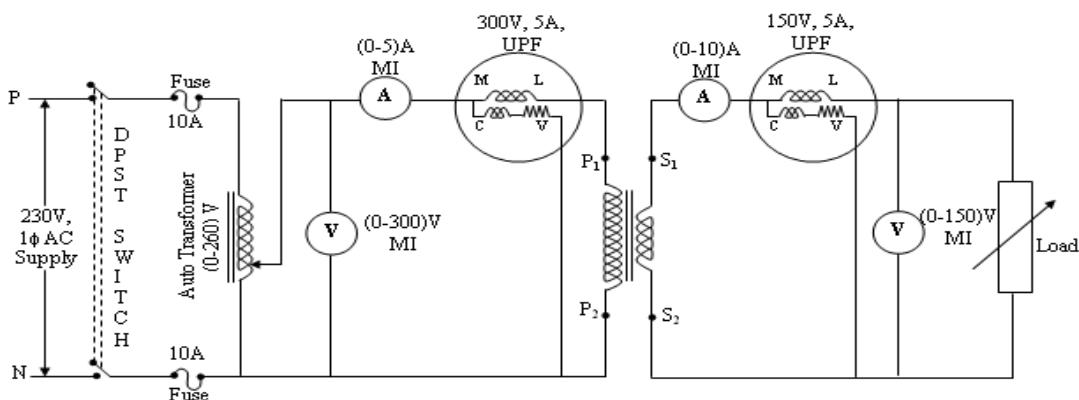

### FUSE RATING:

125% of rated current

$$\frac{125 \times 5}{100} = 6.25\text{A}$$

### NAME PLATE DETAILS:

	<u>Primary</u>	<u>Secondary</u>
Rated Voltage :	230V	115V
Rated Current :	5A	10 A
Rated Power :	1KVA	1KVA

## TABULAR COLUMN:

S.No.	Load	Primary			Secondary			Input Power $W_1 \times MF$	Output Power $W_2 \times MF$	Efficiency $\eta$ %	% Regulation
		$V_1$ (Volts)	$I_1$ (Amps)	$W_1$ (Watts)	$V_2$ (Volts)	$I_2$ (Amps)	$W_2$ (Watts)				

## FORMULAE:

Output Power =  $W_2 \times$  Multiplication factor


Input Power =  $W_1 \times$  Multiplication factor

Output Power

$$\text{Efficiency } \eta \% = \frac{\text{Output Power}}{\text{Input Power}} \times 100\%$$

$$\text{Regulation R \%} = \frac{V_{NL} - V_{FL} (\text{Secondary})}{V_{NL}} \times 100\%$$

### MODEL GRAPHS:

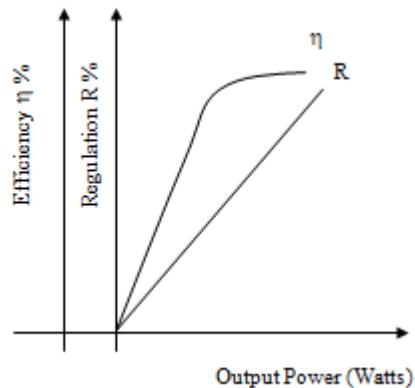

### RESULT:

Thus the load test on single phase transformer is conducted.

<b>Expt. No. 7</b>	<b>OC and SC test on single phase transformer</b>
--------------------	---

### **AIM:**

To conduct load test on single phase transformer and to find efficiency and percentage regulation.

### **APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-10)A (0-5) A	MI MI	1 1
2	Voltmeter	(0-150)V (0-300) V	MI MI	1 1
3	Wattmeter	(300V, 5A) (150V, 5A)	Upf Upf	1 1
4	Auto Transformer	1φ, (0-260)V	-	1
5	Resistive Load	5KW, 230V	-	1
6	Connecting Wires	2.5sq.mm	Copper	Few

### **PRECAUTIONS:**

1. Auto Transformer should be in minimum position.
2. The AC supply is given and removed from the transformer under no load condition.

### **NAME PLATE DETAILS:**

- KVA Rating : :
- Rated H.V side Voltage : :
- Rated H.V side Current : :
- Rated L.V side Voltage : :
- Rated L.V side Current : :

### **FUSE RATING CALCULATIONS:**

The required fuse ratings for O.C. are 20 % of rated current on L.V side

$$= (20/100) \times \text{Rated current on L.V. Side}$$


$$=$$

The required fuse ratings for S.C. are 120 % of rated current on H.V side


$$= (120/100) \times \text{Rated current on H.V. Side}$$

$$=$$

## OPEN CIRCUIT TEST

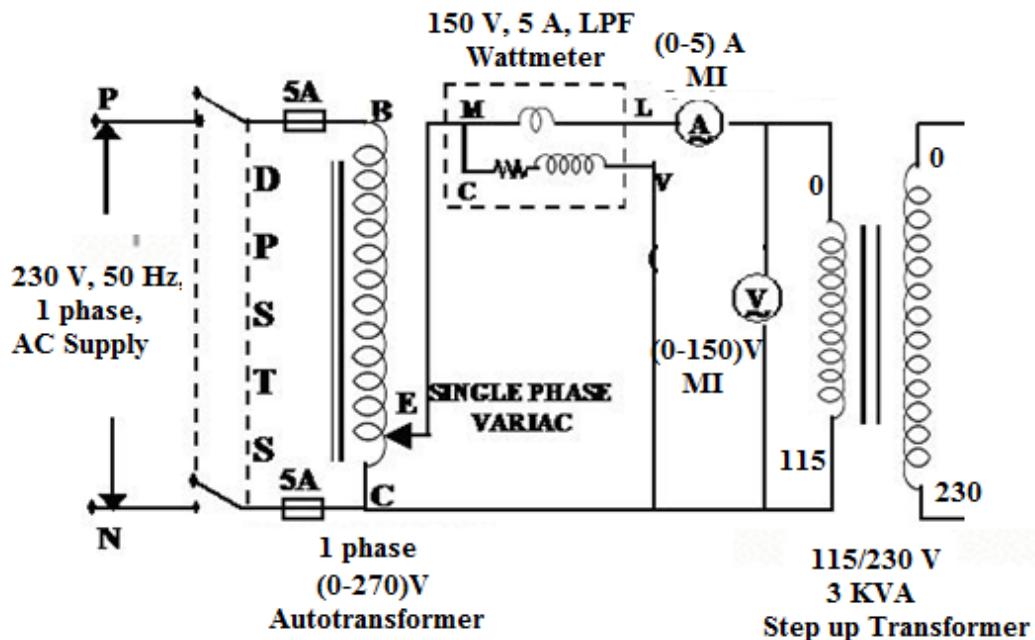

## SHORT CIRCUIT TEST

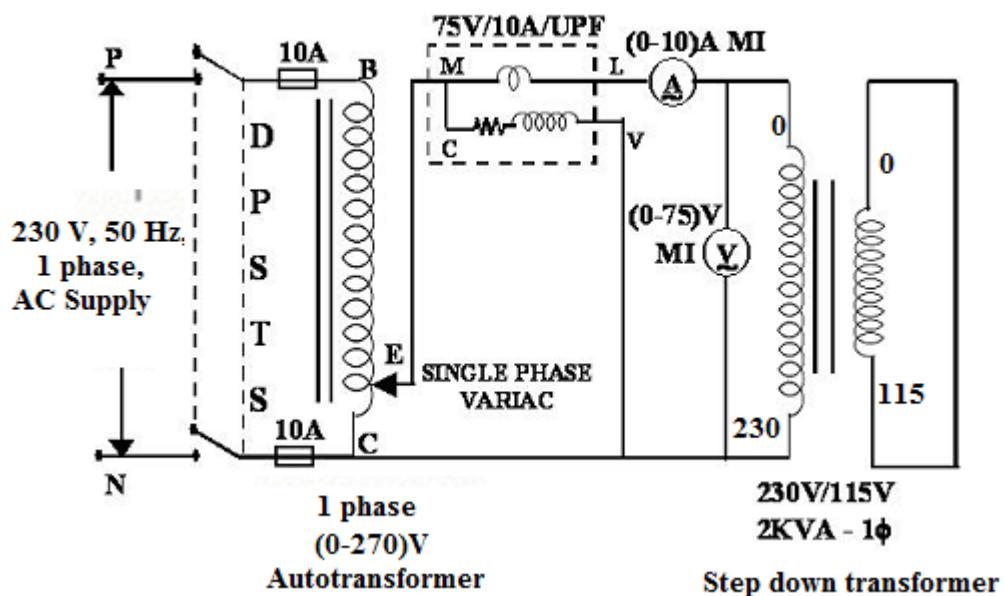

### PROCEDURE:

#### I) O.C. TEST:

1. The circuit connections are made as per the circuit diagram.
2. Keeping the H.V. winding open and the autotransformer in its minimum position the main supply is switched ON.

3. By slowly and carefully adjusting the autotransformer, the rated voltage (115V) is applied to L.V. winding of the transformer.
4. Under this condition the ammeter ( $I_o$ ), Voltmeter ( $V_o$ ) and Wattmeter ( $W_o$ ) readings are noted down.
5. After the experiment is completed, the autotransformer is slowly brought back to minimum position and then the main supply is switched OFF.

## **II) S.C. TEST:**

1. The circuit connections are made as per the circuit diagram.
2. Short circuiting the LV winding and keeping the autotransformer in its minimum position, the main supply is switched ON.
3. By slowly and carefully adjusting the autotransformer the rated current (which is calculated as H.V current.= KVA Rating \*1000 / H.V. is circulated through the H.V. winding.
4. Under this condition, the ammeter ( $I_{SC}$ ), the voltmeter ( $V_{SC}$ ) and the Wattmeter ( $W_{SC}$ ) readings are noted down.
5. After the experiment is completed, the autotransformer is brought back to its minimum position and main supply is switched OFF.

## **TABULATION:**

<b>TEST</b>	<b>VOLTAGE(V)</b>	<b>CURRENT(A)</b>	<b>POWER(W)</b>
O.C TEST (On L.V side)	$V_o =$	$I_o =$	$W_o =$
S.C. TEST (On H.V side)	$V_{SC} =$	$I_{SC} =$	$W_{SC} =$

## **MODEL CALCULATIONS:**

### **1. To obtain the equivalent circuit parameters w.r.t. H.V side**

- i). From the O.C test the; constant loss Iron loss is noted

$$W_c = W_o = \text{_____} \text{ watts.}$$

ii). From the S.C test full load copper loss is noted

$$W_{cu} = W_{sc} = \text{_____ watts.}$$

For a transformer, the equivalent circuit parameters can be determined either w.r.t H.V side or L.V side. If the parameters are estimated on the H.V side ;the resulting equivalent circuit is called H.V side equivalent circuit of the transformer.

**From the O.C test  $R_o$  and  $X_o$  are calculated using the following expressions,**

$$R_o (L.V) = V_o / I_w = \text{Ohms}$$

$$X_o (L.V) = V_o / I_m = \text{Ohms}$$

$$\text{Where } I_w = I_o \cos\theta =$$

$$I_\mu = I_o \sin\theta = \text{and}$$

$$\theta = \cos^{-1}[W_o/V_o I_o] =$$

Since these values are calculated w.r.t L. V side (because O.C test is conducted on the I.V side), the equivalent values of ' $R_o$ ' and ' $X_o$ ' as referred to H.V side are determined as

$$R_o(H.V) = R_o(L.V) / K^2 = \text{&}$$

$$X_o(H.V) = X_o(L.V) / K^2 =$$

$$\begin{aligned} \text{Where } K &= (\text{secondary voltage}) / (\text{primary voltage}) \\ &= 115/230 \text{ for a step down operation.} \\ &= 230/115 \text{ for a step up operation.} \end{aligned}$$

Since we are assuming a step down operation  $k = 115 / 230 = 0.5$ .

$$R_T (H.V) = W_{sc} / I_{sc}^2 =$$

$$Z_T (H.V) = V_{sc} / I_{sc} =$$

$$X_T (H.V) = [Z_T^2 (H.V) - R_T^2 (H.V)]^{1/2} =$$

$R_T$  (H.V) and  $X_T$  (H.V) are the total equivalent resistance and reactance of the transformer as referred to the H.V side whose values are calculated from the S.C test. Now the H.V side equivalent circuit is drawn

## 2. To Predetermine The Efficiency:

The percentage efficiency is then predetermined for different load conditions for a specified load power factor using the expression,

$$\% \text{ Efficiency} = \frac{X^* KVA * \cos\phi * 1000}{(X^* KVA * \cos\phi * 1000) + Wo + X^2 WF.L}$$

When  $X$  is the fraction ;of the full load which is 0.25 for 25% load, 0.5 for 50% load, 0.75 for 75% load, 1.0 for full load and 1.25 for 125% load and  $\cos\phi$  is the load p.f (usually assumed as 0.8 lag) The efficiency valued so calculated are entered in the tabular column as shown. A graph is plotted between percentage efficiency and the output as shown in model graph

## TABULATION:

% Of load  X	Power factor  $\cos\phi$		Power factor  $\cos\phi$	
	0.8	1.0	0.8	1.0
0.25				
0.5				
0.75				
1.0				

% Of load X	Output power = X*KVA*cosφ*100 (watts)		Copper loss = X <sup>2</sup> W <sub>sc</sub> (f.l) (watts)	Total loss = W <sub>c</sub> + copper loss (watts)	Input power = O/p power + losses (watts)		Efficiency% = [(o/p)/(i/p)] x 100 (watts)	
	pf	pf			0.8	1.0	0.8	1.0
	0.8	1.0						
0.25								
0.5								
0.75								
1.0								

### 3. To pre-determine the Percentage Regulation:

The regulation on full load for different leading and lagging power factors are predetermined by formula,

$$\% \text{ Regulation} = \frac{[ I(\text{H.V}) * R_T(\text{H.V}) \cos\phi ] + [ I(\text{H.V}) * X_T(\text{H.V}) \sin\phi ] * 100}{V(\text{H.V})}$$

$$\% \text{ Regulation} = \frac{[ I(\text{H.V}) * R_T(\text{H.V}) \cos\phi ] - [ I(\text{H.V}) * X_T(\text{H.V}) \sin\phi ] * 100}{V(\text{H.V})}$$

Where + for lagging power factor, - for leading power factor.


LH.V = Rated current on H.V side, VH.V = Rated voltage on H.V side. By assuming different leading and lagging power factor such as 0.2, 0.4, 0.6, 0.8 and 1.0 the regulation of the transformer for full load are determined and tabulated as shown below.


### TABULATION:

POWER FACTOR	% Regulation	% Regulation
	For lagging power factor	For leading power factor
0.2		
0.4		
0.6		
0.8		
1.0		

Now a graph is plotted between the percentage regulation and P.F as shown in figure which is known as the regulation graph.

### EQUIVALENT CIRCUIT DIAGRAM:

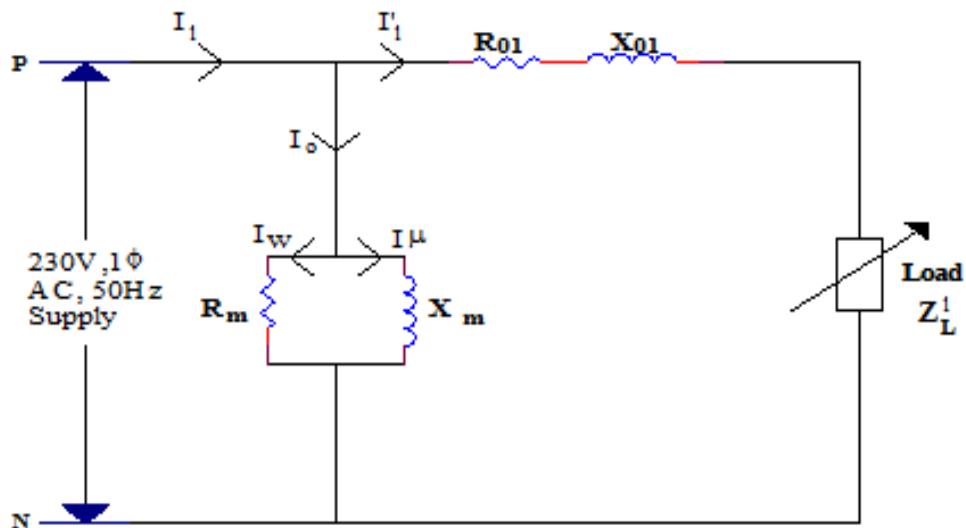

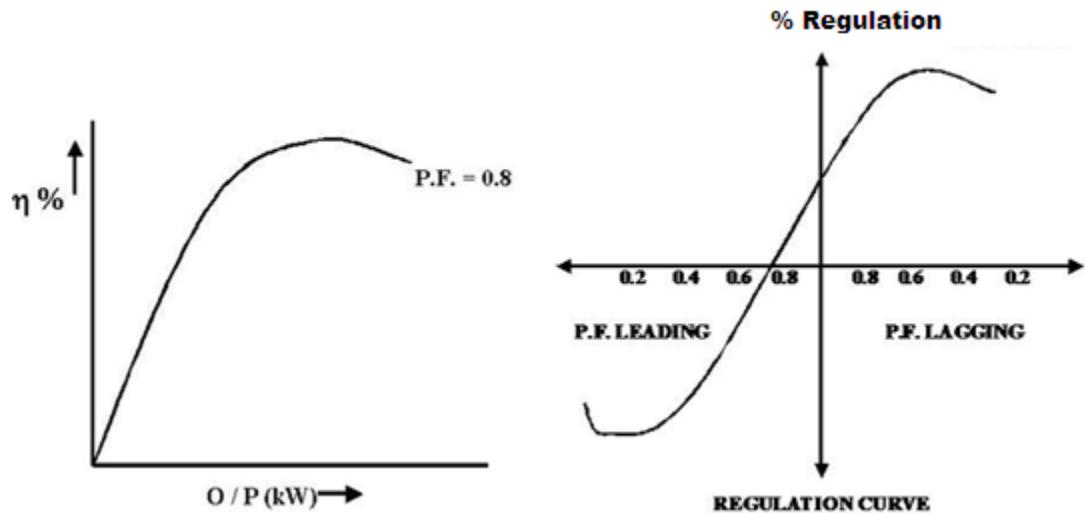

### RESULT:

Thus the O.C and S.C tests are conducted on the single phase transformer and the efficiency and regulation graphs and also the equivalent circuit as referred to H.V side is drawn.

## OC and SC Test

OC

$V_o$	$I_o$	$W_o$ or $P_o$
220V	0.5A	60

SC

$V_{sc}$	$I_{sc}$	$W_{sc}$
12V	4.5A	40

OC Test

$$P_o = V_o I_o \cos \phi_o$$

$$60 = 220 \times 0.5 \cos \phi_o$$

$$\cos \phi_o = \frac{60}{220 \times 0.5} = 0.545$$

$$\phi_o = 56.97^\circ$$

$$I_{\omega} = I_o \cos \phi_o$$

$$= 0.5 \times 0.545$$

$$I_{\omega} = 0.2727 A$$

$$I_m = I_{\omega} \sin \phi_o$$

$$= 0.5 \times \sin(56.97^\circ)$$

$$I_m = 0.419 A$$

$$R_o = \frac{V_o}{I_{\omega}} = \frac{220}{0.2727} = 806.74 \Omega$$

$$X_o = \frac{V_o}{I_m} = \frac{220}{0.419} = 525.059 \Omega$$

$$P_f = 0.2$$

$$\% R = \frac{1.840 \pm 7.48}{230}$$

$$\% R = 4.05\% \text{ (lagging)}$$

$$\% R = -2.45\% \text{ (leading)}$$

$$P_f = 1$$

$$\% R = 4\% \text{ (lagging)}$$

$$\% R = 4\% \text{ (leading)}$$

SC Test

$$P_{SC} = I_{SC}^2 R_{02}$$

$$R_{02} = \frac{P_{SC}}{I_{SC}^2} = \frac{40}{4.5^2} = 1.975 \Omega$$

$$Z_{02} = \frac{V_{SC}}{I_{SC}} = \frac{12}{4.5} = 2.666 \Omega$$

$$X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{2.666^2 - 1.975^2} = 1.790 \Omega$$

$$X_{02} = 1.790 \Omega$$

To predetermine the efficiency:

i)  $\cos \phi = 1 ; \lambda = 1$

$$\text{Copper loss } P_{CV} = X^2 P_{SC}$$

$$= 1^2 \times 40 = 40 \text{ W}$$

$$\text{Core loss } P_0 = 60 \text{ W}$$

$$\text{Total loss } P_L = P_{CV} + P_0$$

$$= 40 + 60$$

$$= 100 \text{ W}$$

$$\text{Output power } P_{out} = \lambda [P_{rated} \cdot \cos \phi] \quad (\because \text{Transformer rating } 1 \text{ kVA})$$

$$= 1 [1000 \times 1]$$

$$P_{out} = 1000 \text{ W}$$

$$\text{Input power } P_{in} = P_{out} + P_L$$

$$= 1000 + 100$$

$$P_{in} = 1100 \text{ W}$$

$$\text{Efficiency } \eta = \frac{P_{out}}{P_{in}} = \frac{1000}{1100} \times 100\% = 90.9\%$$

$$\text{ii) } \cos \phi = 0.8 \Rightarrow \chi = 1$$

$$\text{Copper loss } P_{cv} = I^2 P_{sc}$$

$$= 1^2 \times 40 = 40 \text{ W}$$

$$\text{Core loss } P_c = 60 \text{ W}$$

$$\text{Total loss } P_L = P_{cv} + P_c$$

$$= 40 + 60$$

$$= 100 \text{ W}$$

$$\text{Output Power } P_{out} = \chi [\text{Rated. } \cos \phi]$$

$$= 1 [1000 \times 0.8]$$

$$= 800 \text{ W}$$

$$\text{Input Power } P_{in} = P_{out} + P_L$$

$$= 800 + 100$$

$$= 900 \text{ W}$$

$$\text{Efficiency } \eta = \frac{P_{out}}{P_{in}} = \frac{800}{900} \times 100\% = 88.89\%$$

$$\% \text{ Regulation} = \frac{\bar{I}_1 R_{o1} \cos \phi \pm \bar{I}_1 X_{o1} \sin \phi}{\bar{V}_1} \times 100$$

$$\text{VA rating} = V_1 I_1$$

$$P_{cv} = \bar{I}_1^2 R_{o1}$$

$$Z_{o1} = \frac{V_{sc}}{\bar{I}_1} = \frac{12}{4.34} = 2.76$$

$$Z_{o1} = \sqrt{R_{o1}^2 + X_{o1}^2} = X_{o1}^2 = Z_{o1}^2 - R_{o1}^2$$

$$X_{o1} = 1.76$$

$$R_{o1} = 2.12$$

$$\bar{I}_1 = 4.34$$

$$P_f = 0.8$$

$$\% R = \frac{4.34 \times 2.12 \times 0.8 + 4.34 \times 1.76 \times 0.4}{230}$$

$$= \frac{7.3606 \pm 4.583}{230}$$

$$\% R = 5.19\% \text{ (lagging)}$$

$$\left\{ \frac{7.3606 + 4.583}{230} \right\}$$

$$\% R = 1.207\% \text{ (leading)}$$

$$\left\{ \frac{7.3606 - 4.583}{230} \right\}$$

$$P_f = 0.6$$

$$\% R = \frac{5.52 \pm 6.11}{230}$$

$$\% R = 5.05\% \text{ (lagging)}$$

$$\left\{ \frac{5.52 + 6.11}{230} \right\}$$

$$\% R = -0.25\% \text{ (leading)}$$

$$\left\{ \frac{5.52 - 6.11}{230} \right\}$$

<b>Expt. No. 8</b>	<b>Calculation of Secondary turns and Current in a transformer</b>
--------------------	--

### **AIM:**

To calculate the secondary turns and current in a single phase transformer.

### **APPARATUS REQUIRED:**

<b>SI No.</b>	<b>Apparatus</b>	<b>Range</b>	<b>Quantity</b>
1.	Single phase transformer	230/115 V	1
2.	Auto transformer	0-300V AC	1
3.	Voltmeter	0-300V AC	2
	Ammeter	0-10A AC	1
4.	Connecting wires	-	As required
5.	Single phase AC power supply	-	-

### **THEORY:**

It is essential to know the relative polarity at any instant of primary and secondary terminals for making correct connections. When the two transformers are to be connected in parallel to share the load on the system. The marking is correct if voltage  $V_3$  is less than  $V_1$ , such a polarity is termed as subtractive polarity. The standard practice is to have subtractive polarity because it reduces the voltage stress between adjacent loads. In case  $V_3 > V_1$ , the EMF induced in primary and secondary have additive relation and transformer is said to have additive polarity

### **NAME PLATE DETAILS:**

- KVA Rating : .....
- Rated H.V side Voltage : .....
- Rated H.V side Current : .....
- Rated L.V side Voltage : .....
- Rated L.V side Current : .....

### **FUSE RATING CALCULATIONS:**

The required fuse ratings for O.C. are 20 % of rated current on L.V side

$$= \quad (20/100) \times \text{Rated current on L.V. Side}$$


$$=$$

The required fuse ratings for S.C. are 120 % of rated current on H.V side

$$= (120/100) \times \text{Rated current on H.V. Side}$$

=

### CIRCUIT DIAGRAM:

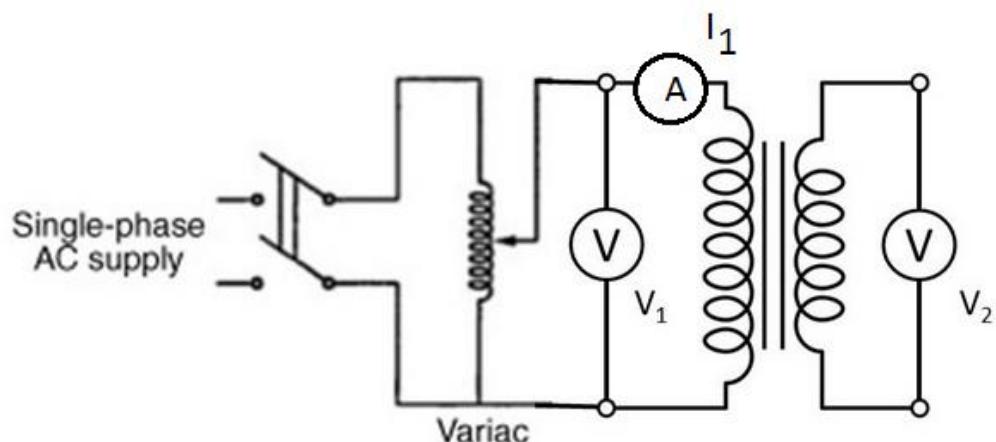

### PROCEDURE:

1. Connect the circuit as shown in the diagram.
2. Switch on the a.c. supply.
3. Record voltage  $V_1$  across primary and  $V_2$  across various tappings of secondary.
4. If  $V_1 > V_2$  then transformer is step down.
5. If  $V_2 > V_1$  then transformer is step up.
6. Switch off a.c. supply

**TABULAR COLUMN:**

S.NO	Primary Voltage (V1) in volts	Secondary voltage (V2) in volts	Primary Current (I1) in amps	Turn ratio (k=V1/V2)	Secondary current, I2=I1/k

**RESULT:**

Thus the transformation ratio and the secondary current are measured for a given single phase transformer.

## 9. LOAD TEST ON SINGLE PHASE INDUCTION MOTOR

### AIM:

To conduct load test on the given single phase induction motor and to plot its performance characteristics.

(i) Electrical characteristics – speed, torque, slip, power factor and efficiency vs. output power

### APPARATUS REQUIRED:

S.NO	APPARATUS	SPECIFICATIONS	QUANTITY
1	VOLTMETER	(0-300V) MI	1
2	AMMETER	(0-10A) MI	1
3	WATTMETER	(300V,10A,UPF)	1
4	TACHOMETER	(0-10000 RPM)	1

### FORMULAE:

$$1. \text{ circumference of the brake drum} = 2\pi R \text{ (m)}$$

R = Radius of the brake drum

$$2. \text{ Input power } W \text{ (watts)}$$

W = wattmeter readings

$$3. \text{ Torque (T)} = 9.81 * R * (S_1 - S_2) \text{ (N-m)}$$

S<sub>1</sub>, S<sub>2</sub> = spring balance readings (Kg)

$$4. \text{ Output power} = \frac{2\pi NT}{60} \text{ (watts)}$$

N- Speed in rpm

$$5. \% \text{ Efficiency} (\eta) = \frac{\text{output power}}{\text{input power}} \times 100$$

$$6. \text{ Power factor, COS } \Phi = \frac{W}{VI}$$

$$7. \% \text{ Slip, } S = \frac{N_s - N}{N_s} \times 100$$

$$N_s = \text{synchronous speed} = \frac{120f}{P} \text{ (rpm)}$$

P = no. of poles

F=frequency of supply (Hz)

## **PRECAUTIONS:**


1. The auto transformer is kept at minimum voltage position.
2. The motor is started at no load condition.


## **PROCEDURE:**

1. Connections are as per the circuit diagram
2. The DPST switch is closed and the single phase supply is given
3. By adjusting the VARIAC the rated voltage is applied and the corresponding no load values of speed, spring balance and meter readings are noted down. If any of the wattmeter readings shows negative on no load or light loads, switch off the supply & interchange the terminals of pressure coils/current coils (not both) of that wattmeter.  
Now, again starting the motor (follow above procedure for starting), take readings.
4. The procedure is repeated till rated current of the machine.
5. The motor is unloaded, the auto transformer is brought to the minimum voltage position, and the DPSTS is opened.
6. The radius of the brake drum is measured.

### TABULAR COLUMN:

V volts	I Amps	Speed N (rpm)	Wattmeter reading	Spring readings			balance $T = 9.81 * R$ $* (S_1 - S_2)$	output power O/P = $2 \text{ INT} / 60$	Power factor $\cos \Phi$	% efficiency $\eta = OP/IP$	Slip = $S = N_s - N / N_s * 100\%$
				S1	S2	S1-S2					
220	6.2	1470	OBS	40	160	0	0	0	0	0	0.02
220	6.5	1460	ACT	130	520	0.6	2.6	2	2.23	341.84	0.364
218	7.0	1450	OBS	180	720	0.8	3.4	2.6	2.90	441.34	0.472
218	7.5	1440	ACT	220	880	1.0	4.2	3.2	3.78	570.78	0.538
218	8.0	1430	OBS	250	1000	1.2	5.4	4.2	4.97	743.88	0.573
216	8.5	1420	ACT	290	1160	1.4	5.8	4.4	5.20	773.90	0.632
216	9.0	1410	OBS	315	1260	1.6	6.2	4.6	5.44	803.43	0.648
214	9.5	1400	ACT	350	1400	1.8	6.8	5	5.91	867.04	0.689

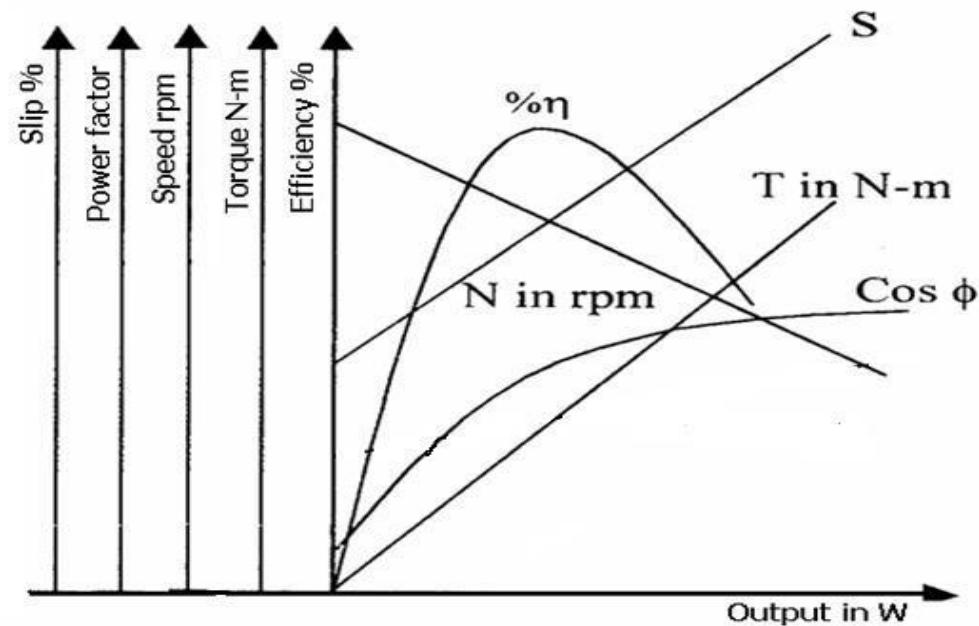**MODEL GRAPH:**

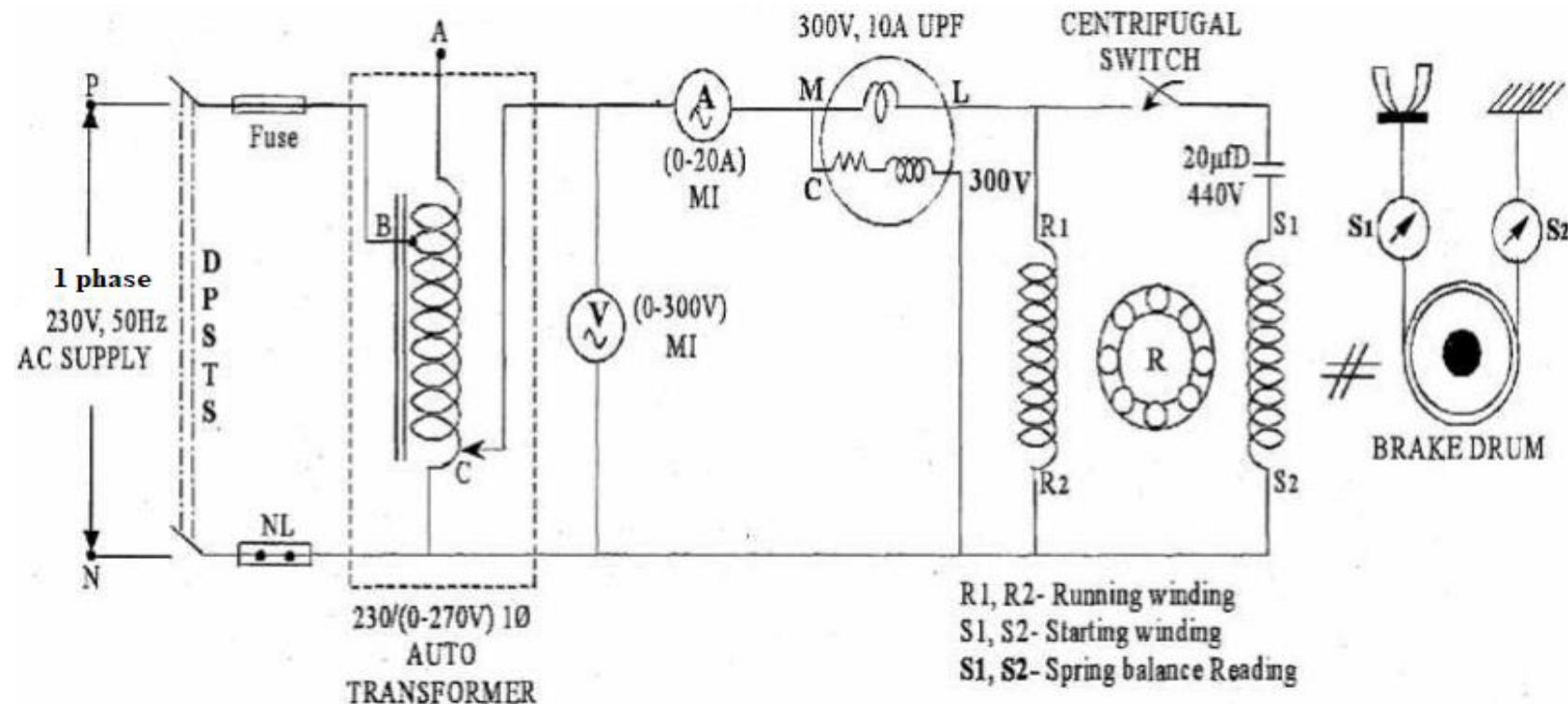**CIRCUIT DIAGRAM: LOAD TEST ON SINGLE PHASE INDUCTION MOTOR**

**FUSE RATING:**

125% of rated current

$$\begin{aligned} 125 \times 9.5 \\ \hline = 15 \text{ A} \end{aligned}$$

100

**NAME PLATE DETAILS:**

Rated Voltage :	220V
Rated Current :	9.5A
Rated Power :	3HP
Rated Speed :	1470 RPM

S1, S2- AUXILIARY WINDING  
M1, M2- MAIN WINDING

<b>Theoretical Calculations</b>	<b>20</b>	
<b>Observation</b>	<b>20</b>	
<b>Execution of practice examples</b>	<b>30</b>	
<b>Viva</b>	<b>10</b>	
<b>Record</b>	<b>20</b>	
<b>Total Score</b>	<b>100</b>	
<b>Date of experiment</b>		
<b>Date of record submission</b>		<b>Faculty signature</b>

**RESULT:**

The load test was conducted on 1Φ induction motor and the performance characteristics were drawn.


<b>Expt. No. 10</b>	<b>Output Characteristics of LVDT</b>
---------------------	---------------------------------------

**AIM:**

To plot the output characteristics of LVDT.

**APPARATUS REQUIRED:**


S.No.	Apparatus	Quantity
1	LVDT kit	1
2	Multimeter	1
3	Connecting Wires	As required

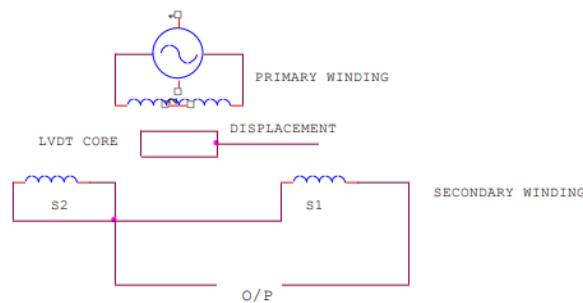**CIRCUIT DIAGRAM:**

**PROCEDURE:**

1. Connect the circuit according to circuit diagram.
2. Switch on the power supply.
3. The core is initially brought to null position.
4. First turn the nut in clockwise direction to move core inwards i.e. left of null position & take respective voltage readings on the voltmeter.
5. Now turn nut in anticlockwise direction to move the core towards right of null point & again take respective voltage reading from voltmeter.
6. Plot the graph from the observations taken.

**TABULAR COLUMN:**

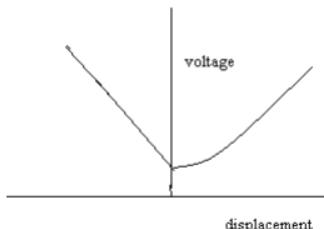Direction of displacement	Displacement (mm)	Voltage (V)

**MODEL GRAPH:**


**RESULT:** Thus the output characteristics of LVDT is plotted.

**Expt. No. 11**

**Three phase Power measurement using Two Wattmeter method**


**AIM:**

To measure the power in three phase balanced star connected load using two wattmeter method.

**APPARATUS REQUIRED:**

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-10)A	MI	1
2	Voltmeter	(0-600) V	MI	1
3	Wattmeter	(600V, 10 A)	Lpf	2
4	Auto Transformer	3φ, (0-600)V	-	1
5	Lamp load	-	-	1
6	Connecting Wires	2.5sq.mm	Copper	Few

**CIRCUIT DIAGRAM**

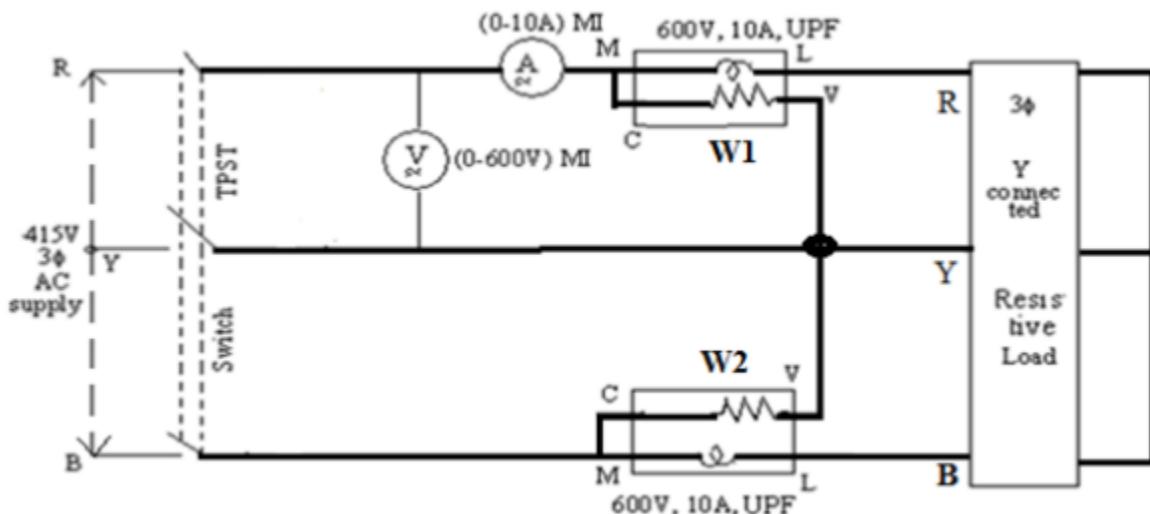

**PROCEDURE:**

1. Make the connections as per the circuit diagram shown in Fig 5.1.
2. Switch ON 3 phase AC supply.
3. Apply load and measure the values of wattmeters, ammeter and voltmeter.
4. Switch OFF all the loads and supply.

**TABULAR COLUMN:**

Sl No.	Line voltage $V_L$ (V)	Line current $I_L$ (A)	Wattmeter (W1)	Wattmeter (W2)	$W = W_1 + W_2$	Calculated power (W)

**MODEL CALCULATIONS:**

1. Total Power,  $P = W_1 + W_2$  Watts.
2. Power Factor  $\text{Cos } \phi = \text{Cos} [ \tan^{-1} \{ \sqrt{3} ( W_1 - W_2 ) / ( W_1 + W_2 ) \} ]$
3. Calculated Power  $= \sqrt{3} V_L I_L \text{Cos} \phi$

**RESULT:**

Thus, the power in three phase balanced star connected load using two wattmeter method is measured and calculated.

<b>Expt. No. 12</b>	<b>Energy consumption measurement using a Single Phase Energy Meter</b>
---------------------	---


### AIM:

To measure the energy consumption using single phase energy meter.

### APPARATUS REQUIRED:

S.No.	Apparatus	Range	Type	Quantity
1	Ammeter	(0-20)A	MI	1
2	Voltmeter	(0-300) V	MI	1
3	Auto Transformer	1φ, (0-270)V	-	1
4	Lamp load	-	-	1
5	Connecting Wires	2.5sq.mm	Copper	Few

### CIRCUIT DIAGRAM

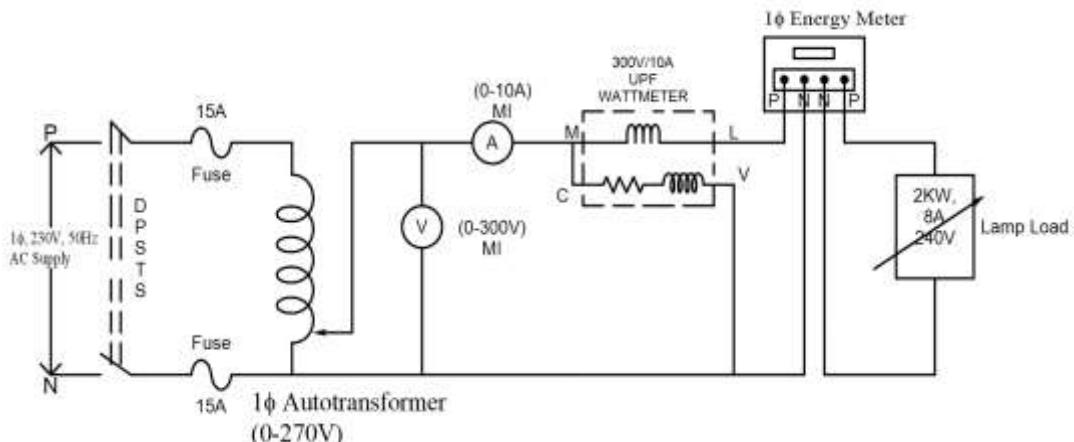

### PROCEDURE:

1. Connect the circuit as shown in circuit diagram.
2. Connect the load rheostat  $10 \Omega/12A$  in series with load.
3. Keep the variac in minimum output voltage position.
4. Keep the load in maximum position.
5. Adjust the variac output equal to the rated voltage of energy meter.
6. Adjust the load till rated current of energy meter passes through it.
7. Note down the voltmeter and ammeter readings.
8. Note down the time taken for 2 revolutions of disc in the energy meter.
9. Switch off the supply.
10. Repeat the above steps for different currents.

**TABULAR COLUMN:**

Sl No.	Line voltage V <sub>L</sub> (V)	Line current I <sub>L</sub> (A)	Time taken for 2 revolutions (sec)	No.of revolutions (n)	Calculated Energy (Whr)	Measured Energy (Whr)

**MODEL CALCULATIONS:**

1. Calculated energy consumed during 'n' revolutions  $W_a = V \cdot I \cdot t / 3600 =$  (watt-hour)  
where V= Voltage (V)  
I= Current (A)  
t = Time (S)
2. Measured Energy by energy meter  $W_R = n / \text{meter constant}$

**RESULT:**

Thus the energy consumption using single phase energy meter is measured.

<b>Expt. No. 13</b>	<b>Load test on DC shunt motor</b>
---------------------	------------------------------------

### **AIM:**

To conduct the brake load test on DC shunt motor and determine its performance characteristics.

### **APPARATUS REQUIRED:**

S.No:	Name of the Apparatus	Range	Type	Quantity
1	Ammeter	(0-20)A	Digital	1
2	Voltmeter	(0-300)V	Digital	1
3	Rheostat	370 /1.7A	Wire Wound	1
4	RPM meter	(0-9999) rpm	Digital	1
5	Connecting Wires	-	-	As Required

### **THEORY:**

It is a direct method in which a braking force is applied to a pulley mounted on the motor shaft. A belt is wound round the pulley and its two ends are attached to the frame through two spring balances S1 and S2. The tension of the belt can be adjusted with the help of tightening wheels. The tangential force acting on the pulley is equal to the difference between the readings of the two spring balances.

Spring balance readings are S1 and S2 in Kg.

Radius of the shaft is R in meters.

Speed of the motor is N in rpm.

Input voltage across the motor is V in volts

Input current is I in amps


$$\text{Torque (T)} = (S1 - S2) R \times 9.81 \text{ in N-m.}$$

$$\text{Motor output} = 2\pi NT/60 \text{ in Watts}$$

$$\text{Motor input} = VI \text{ in Watts}$$

$$\text{Efficiency} = \text{Output/ Input} = 2\pi NT / 60 (VI)$$

## CIRCUIT DIAGRAM:

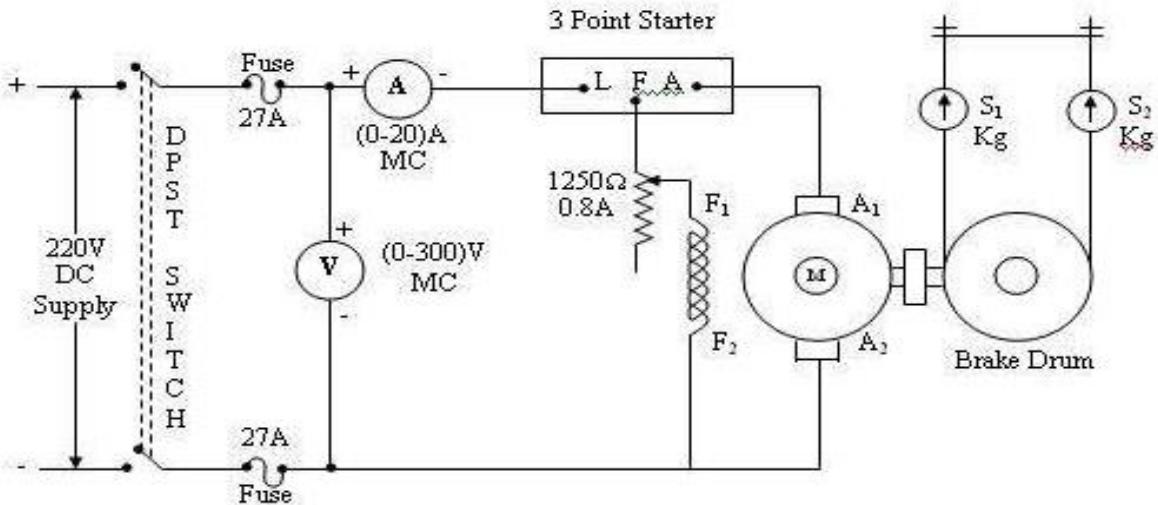

### FUSE RATING:

$$\begin{aligned} & \text{125\% of rated current} \\ & \frac{125 \times 21}{100} = 26.25\text{A} \end{aligned}$$

### NAME PLATE DETAILS:

Rated Voltage : 220V  
 Rated Current : 21A  
 Rated Power : 3.5KW  
 Rated Speed : 1500 RPM

## PROCEDURE:

1. Make the connections as shown in the circuit diagram.
2. Keeping the field rheostat ( $R_f$ ) at the minimum position, switch on the supply and start the motor.
3. Adjust the speed of the motor on no load to its rated value by means of the field rheostat. Do not disturb the position of the rheostat throughout the test.
4. Put on the load by tightening the screws of the spring balances. Note down the spring tensions, the speed, the voltage and the currents at different loads until full load current obtained.

## CALCULATIONS:

1. Measure the circumference of the brake drum and calculate its radius ( $r$ ), in meters.

- Torque (T) =  $9.81 (S_1 - S_2) \cdot r$

Where,  $S_1, S_2 \rightarrow$  Spring balance readings in kg

$r \rightarrow$  Radius of brake drum in m

9.81 → Constant to convert kg to Newton

2. Output Power ( $P_{out}$ ) =  $2\pi NT/60$

Where N= Speed in rpm

3. Input power ( $P_{in}$ ) =  $V_L \cdot I_L$  Watts

$V_L$ =Input voltage in volts

$I_L$ =Input current in Amps

4. % Efficiency =  $(P_{out}/P_{in}) * 100$

#### TABULAR COLUMN:

Circumference of Brake Drum = 60cm

S.N o.	Voltage	Current	Speed in rpm	Spring Balance		$F = (S_1 - S_2) \times 9.81$	Torqu e (NM)	Output Power (W)	Input Power (W)	Efficiency $\eta$ in (%)
				$S_1$	$S_2$					
1.	210	1.2	1532	0	0	0	-	-	-	-
2.	210	2.2	1500	4	1	29.43	3.4	441.43	462	95.54
3.	208	7.1	1480	8	2	58.86	6.7	871.04	1476	59.01
4.	200	9	1450	10	3	68.67	7.8	995.74	1800	55.32
5.	200	10.6	1400	12	3	88.29	10.1	1236	2120	59.24
6.	200	12	1380	13	3	98.1	11.2	1353.6	2400	56.4

#### Theoretical Calculations:

$$\text{Circumference } C = 2\pi R = 2 \times 3.14 \times R$$

$$F = (S_1 - S_2) \times 9.81$$

$$F = (4-1) \times 9.81 = 29.43$$

$$F = (8-2) \times 9.81 = 58.86$$

$$F = (10-3) \times 9.81 = 68.67$$

$$F = (12-3) \times 9.81 = 88.29$$

$$F = (13-3) \times 9.81 = 98.1$$

$$R = \frac{C}{2\pi} = \frac{60 \times 10^{-2}}{2 \times 3.14} = 0.09554$$

$$\text{Torque} = F \times R$$

$$T = 29.43 \times 0.09554 = 2.8117$$

$$T = 58.86 \times 0.09554 = 5.623$$

$$T = 68.67 \times 0.09554 = 6.561$$

$$T = 88.29 \times 0.09554 = 8.435$$

$$T = 98.1 \times 0.09554 = 9.372$$

$$\text{Output Power} = \frac{2\pi NT}{60}$$

$$\text{Output Power } P_o = \frac{2 \times 3.14 \times 1500 \times 2.8117}{60} = 441.4369W$$

$$\text{Output Power } P_o = \frac{2 \times 3.14 \times 1480 \times 5.623}{60} = 871.04W$$

$$\text{Output Power } P_o = \frac{2 \times 3.14 \times 1450 \times 6.561}{60} = 995.74W$$

$$\text{Output Power } P_o = \frac{2 \times 3.14 \times 1400 \times 8.435}{60} = 1236W$$

$$\text{Output Power } P_o = \frac{2 \times 3.14 \times 1380 \times 9.372}{60} = 1353.69W$$

$$\text{Input Power } P_{in} = V \cdot I$$

$$\text{Input Power } P_{in} = 210 \times 2.2 = 462W$$

$$\text{Input Power } P_{in} = 208 \times 7.1 = 1476.8W$$

$$\text{Input Power } P_{in} = 200 \times 9 = 1800W$$

$$\text{Input Power } P_{in} = 200 \times 10.6 = 2120W$$

$$\text{Input Power } P_{in} = 200 \times 12 = 2400W$$

$$\text{Efficiency } \eta = \frac{\text{Output Power}}{\text{Input Power}}$$

$$\text{Efficiency } \eta = \frac{441.436}{462} = 95.54\%$$



$$\text{Efficiency } \eta = \frac{871.04}{1476} = 59.01\%$$



$$\text{Efficiency } \eta = \frac{995.74}{1800} = 55.32\%$$

$$\text{Efficiency } \eta = \frac{1256}{2120} = 59.24\%$$

$$\text{Efficiency } \eta = \frac{1353.69}{2400} = 56.4\%$$

### MODEL GRAPH:

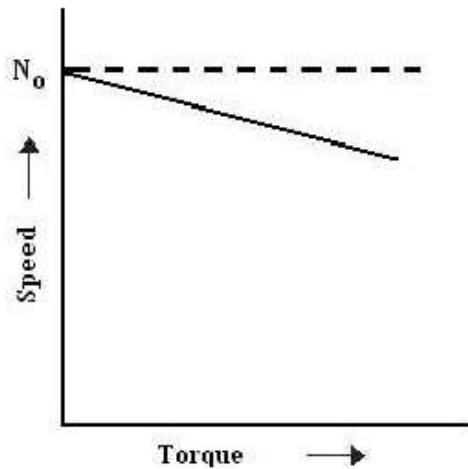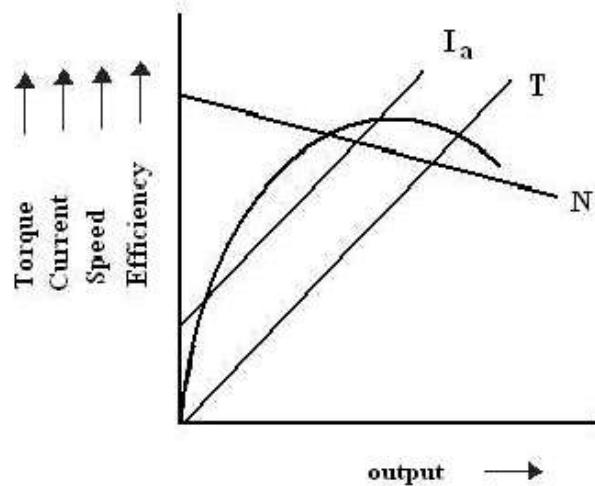

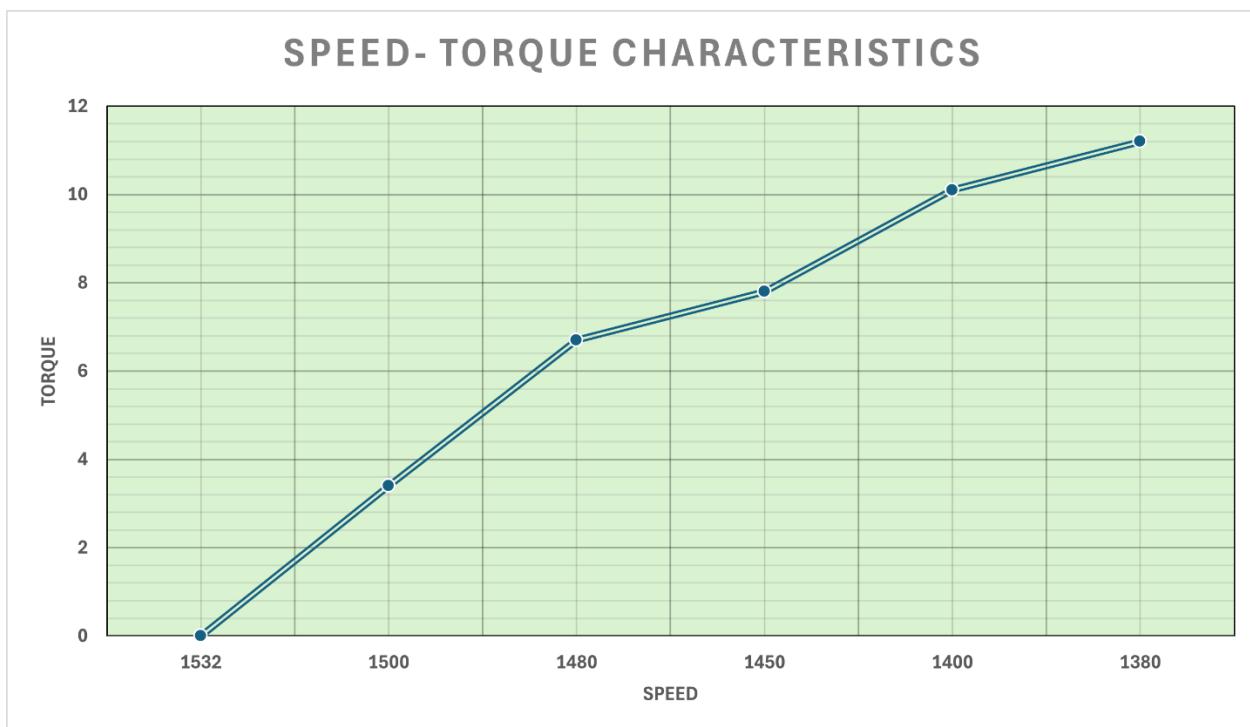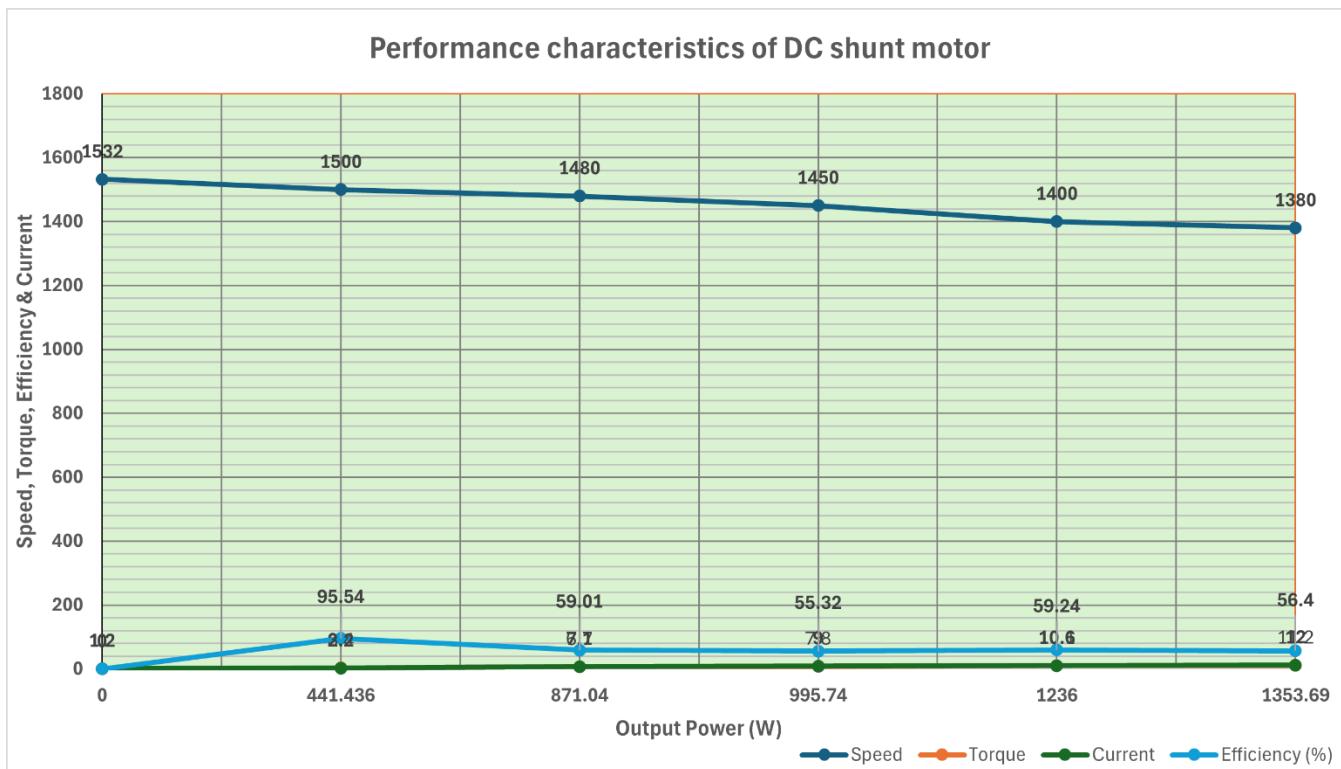

## RESULT:

Thus the performance characteristics of DC shunt motor was obtained by conducting brake test.

Expt. No. 14(a)	Staircase Wiring

### Staircase Wiring

#### **AIM:**


To control the status of the given lamp using two-way switches.

#### **APPARATUS REQUIRED:**

S.NO	APPARATUS	RANGE / TYPE	QUANTITY
1	Incandescent Lamp	60W/40W	1
2	SPDT (Single Pole Double Throw-Double Way Switch)	5A, 230V	2
3	Lamp holder	Pendant type	1
4	Line Tester	500V / Taparia 813	1
5	3 Pin Plug	5A, 230V	1
6	Wire Stripper Cum Cutter	Pye 950	1
7	Connecting Wires	12A / 1 sq.mm Area/ 0.7 Thickness	As Per Requirement
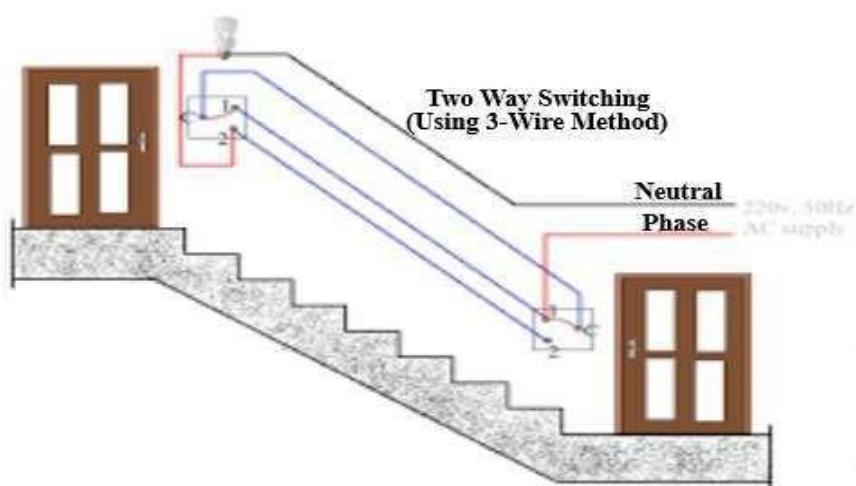
#### **THEORY:**

Staircase wiring is a common multi-way switching or two-way light switching connection; one light two switches wiring. One lamp is controlled by two switches from two different positions that is to operate the load from separate positions such as above or below the staircase, from inside or outside of a room, or as a two-way bed switch. The main purpose of two-way switching connection is to connect and control AC appliances and equipments from two separate locations. It is mostly used in staircase wiring where a light bulb can be controlled (Switch ON / Switch OFF) from different places, no matter you are in the upper or lower portion of stair; it does not depend on the switches position as well. You just have to press the switch button to OFF/ON to perform the switching operation. It is also used in rooms having large area which has two entry and exit gates. It is used to control any electrical (AC or DC) appliance or equipment like fan, light bulbs etc from two different places.




### **PROCEDURE:**


1. A piece of wire is connected to the phase side and other end to the middle point of SPDT switch1.
2. Another point of lamp holder is connected to neutral line.
3. Upper point of SPDT switch 1 is connected to the upper point of SPDT switch 2.Lower point of SPDT switch 1 is connected to the lower point of switch 2.
4. Circuit is tested that all combination of switch connection.

### **CIRCUIT DIAGRAM:**

#### **DIRECT CONNECTION:**

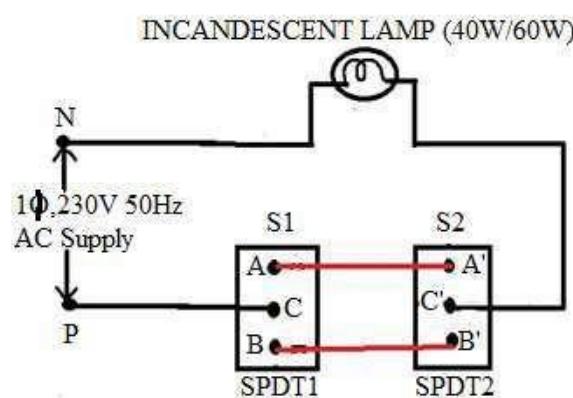

#### **INDIRECT CONNECTION:**

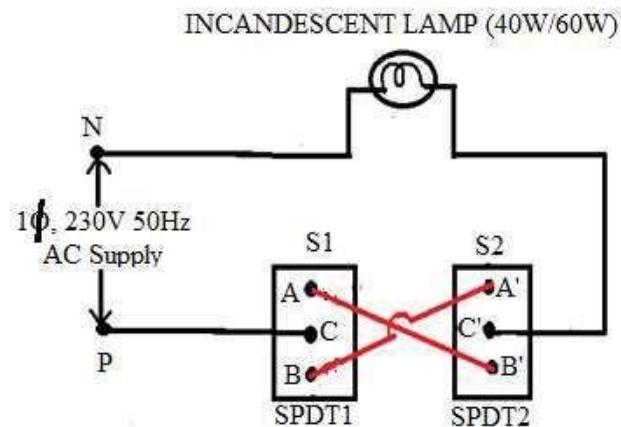

### **TABULATION:**

#### **DIRECT CONNECTION:**

S.NO	S1	S2	LAMP STATUS
1	CA	C'A'	ON
2	CB	C'B'	ON
3	CA	C'B'	OFF
4	CB	C'A'	OFF

#### **INDIRECT CONNECTION:**

S.NO	S1	S2	LAMP STATUS
1	CA	C'A'	OFF
2	CB	C'B'	OFF
3	CA	C'B'	ON
4	CB	C'A'	ON

### **RESULT:**

Thus the status of the given lamp was controlled and tested under direct and indirect connection using two way switches.

<b>Expt. No. 14(b)</b>	<b>Fluorescent tube wiring</b>

### **AIM:**

To prepare wiring for a fluorescent tube light with switch control.

### **APPARATUS REQUIRED:**

<b>SI No.</b>	<b>Apparatus</b>	<b>Range</b>	<b>Quantity</b>
1.	Tube light with fitting	-	1
2.	Joint clips	-	As required
3.	Switch	-	1
4.	Wires	-	As required
5.	Screws	-	As required
6.	Switch board	-	1

### **THEORY:**


#### **Working of the Fluorescent Tube Light:**

The fluorescent lamp circuit consists of a choke, a starter, a fluorescent tube and a frame. The length of the commonly used fluorescent tube is 100 cm; its power rating is 40 W and 230V. The tube is filled with argon and a drop of mercury. When the supply is switched on, the current heats the filaments and initiates emission of electrons. After one or two seconds, the starter circuit opens and makes the choke to induce a momentary high voltage surge across the two filaments. Ionization takes place through argon and produces bright light.

### **PROCEDURE:**

1. Mark the switch and tube light location points and draw lines for wiring on the wooden board.
2. Place wires along the lines and fix them with the help of clips.
3. Fix the switch and tube light fitting in the marked positions.
4. Complete the wiring as per the wiring diagram.
5. Test the working of the tube light by giving electric supply to the circuit.

### CIRCUIT DIAGRAM - TUBE LIGHT

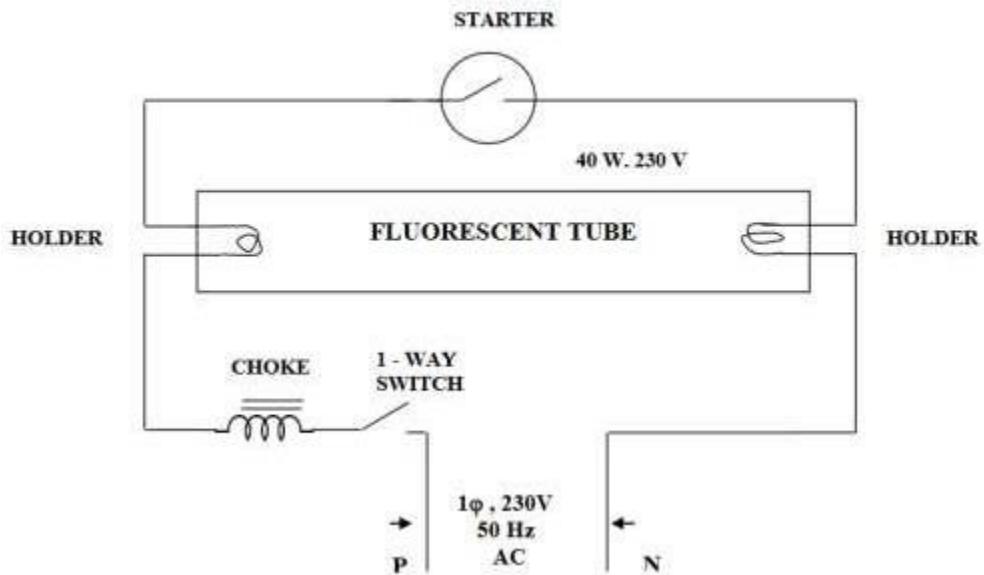

#### **INFERENCE:**

When SW is switched on:

CONDITION	OBSERVATION
With Starter	

If the starter is removed with the tube light on, \_\_\_\_\_

#### **RESULT:**

Thus the wiring for the tube light is completed and tested.

## Exp: 15 FIND STABILITY OF A SYSTEM USING ROUTH HURWITZ CRITERION

### Aim:

To determine the stability of the closed-loop system using Routh Hurwitz Criterion for the given polynomial characteristics equations.

- (i)  $(s)=s^4+2s^3+3s^2+4s+5$  and
- (ii)  $(s)=s^5+7s^4+6s^3+42s^2+8s+56$

### Tools Used:

- (i) SCILAB software
- (ii) PC

### Program code:

```
clear;
clc;
xdel(winsid());
mode(0);
s=%s;
H=s^4+2*s^3+3*s^2+4*s+5;
//H=s^5+7*s^4+6*s^3+42*s^2+8*s+56;
disp(H,'The given characteristics equation 1-G(s)H(s)=');
c=coeff(H);
len=length(c);
r=routh_t(H);
disp(r,"Rouths table=");
x=0;
for i=1:len
if(r(i,1)<0)
x=x+1;
end
end
if(x>=1)
printf("From Rouths table, it is clear that the system is unstable.")
else
printf("From Rouths table, it is clear that the system is stable.")
end
```

### Simulation output:

```
Scilab 6.0.2 Console

The given characteristics equation 1-G(s)H(s)=

      2   3   4
5 +4s +3s +2s +s

Rouths table=

 1.   3.   5.
 2.   4.   0.
 1.   5.   0.
-6.   0.   0.
 5.   0.   0.

From Rouths table, it is clear that the system is unstable.
--> |
```

```
Scilab 6.0.2 Console

The given characteristics equation 1-G(s)H(s)=

      2   3   4   5
56 +8s +42s +6s +7s +s

Rouths table=

 1.       6.     8.
 7.       42.    56.
 28.      84.    0.
 21.      56.    0.
 9.3333333 0.    0.
 56.      0.    0.

From Rouths table, it is clear that the system is stable.
--> |
```

Marks Obtained:

<b>Theoretical Calculations</b>	<b>20</b>	
<b>Observation</b>	<b>20</b>	
<b>Execution of practice examples</b>	<b>30</b>	
<b>Viva</b>	<b>10</b>	
<b>Record</b>	<b>20</b>	
<b>Total Score</b>	<b>100</b>	
<b>Date of experiment</b>		
<b>Date of record submission</b>		<b>Faculty signature</b>

### RESULT:

Thus the stability of a system using routh hurwitz criterion is verified.

<b>EX NO:17</b>	
<b>DATE:</b>	Generation of Common Discrete Time Signals

### Aim

Generate and plot the Unit Impulse Signal, Unit Step Signal, Unit Ramp Signal, Sinusoidal Signal, Exponential Signal: For each signal Write the SCILAB code to generate the signal. Plot the signal and label the axes appropriately.

### using SCILAB:

**Unit Impulse Signal, Unit Step Signal, Unit Ramp Signal, Sinusoidal Signal, Exponential Signal: For each signal** Write the SCILAB code to generate the signal. Plot the signal and label the axes appropriately.

### Software Required

1. Scilab 6.1.0

### Procedure:

- Start the scilab Program
- Open scinotes , type the program and save the program in current directory
- Compile and run the program
- If any error occur in the program, correct the error and run the program
- For the output , see the console window
- Stop the program

### Theory:

Discrete-time signals are a fundamental concept in digital signal processing and communication. They represent variations in amplitude over discrete points in time. Here, I'll provide a brief overview of some common discrete-time signals and their characteristics:

**Unit Step Signal ( $u[n]$ ):** The unit step signal is a basic discrete-time signal that takes the value 1 for non-negative time indices ( $n \geq 0$ ) and 0 otherwise. It is often used to model the onset of events or changes in a system.

**Impulse Signal ( $\delta[n]$ ):** The impulse signal is also known as the discrete-time delta function. It has a value of 1 at  $n = 0$  and is zero for all other time indices. It's a

fundamental signal in signal processing and is used to represent discrete-time impulses or impulses in discrete-time systems.

Exponential Signal: An exponential discrete-time signal is defined as  $x[n] = A * \alpha^n$ , where  $A$  is the amplitude and  $\alpha$  is the exponential factor. Depending on whether  $\alpha$  is greater or less than 1, the signal can grow or decay exponentially with time.

Sinusoidal Signal: A sinusoidal discrete-time signal has the form  $x[n] = A * \cos(\omega n + \phi)$ , where  $A$  is the amplitude,  $\omega$  is the angular frequency,  $n$  is the time index, and  $\phi$  is the phase shift. Sinusoidal signals exhibit periodic behavior and are a fundamental representation of oscillations.

Ramp Signal: A ramp signal is a linearly increasing or decreasing signal with time. It's given by  $x[n] = a * n$ , where ' $a$ ' is the slope of the ramp. The ramp signal is commonly used to model linear changes or trends.

Random Signal: A random signal represents random variations or noise in a system. It's often generated using a random number generator. In digital communication, noise can introduce errors in the received signal, impacting the quality of communication.

### **Program:**

```
//UNIT IMPULSE SIGNAL
clear all;
close ;
N=5; //SET LIMIT
t1 = -5:5;
x1 =[ zeros (1 , N ) ,ones (1 ,1) ,zeros (1 , N ) ];
subplot (2 ,4 ,1);
plot2d3 ( t1 , x1 )
xlabel ( ' tim e ' );
ylabel ( ' Ampli tude ' );
title ( ' Uni t im p ul s e s i g n a l ' );
//UNIT STEP SIGNAL
t2 = -5:5;
x2 =[ zeros (1 , N ) ,ones (1 , N +1) ];
subplot (2 ,4 ,2);
plot2d3 ( t2 , x2 )
xlabel ( ' tim e ' );
ylabel ( ' Ampli tude ' );
title ( ' Uni t s t e p s i g n a l ' );
//EXPONENTIAL SIGNAL
t3 =0:1:20;
```


```

x3 =exp( - t3 ) ;
subplot (2 ,3 ,3) ;
plot2d3 ( t3 , x3 ) ;
xlabel ( ' time ' ) ;
ylabel ( ' Amplitude ' ) ;
title ( ' Exponential signal ' ) ;

//UNIT RAMP SIGNAL 4
t4 =0:20;
x4 = t4 ;
subplot (2 ,3 ,4) ;
plot2d3 ( t4 , x4 ) ;
xlabel ( ' time ' ) ;
ylabel ( ' Amplitude ' ) ;
title ( ' Unit ramp signal ' ) ;
//SINUSOIDAL SIGNAL
t5 =0:0.04:1;
x5 =sin (2* %pi * t5 ) ;
subplot (2 ,3 ,5) ;
plot2d3 ( t5 , x5 ) ;
title ( ' Sinusoidal signal ' ) ;
xlabel ( ' time ' ) ;
ylabel ( ' Amplitude ' ) ;
//RANDOM SIGNAL
t6 = -10:1:20;
x6 = rand (1 ,31) ;
subplot (2 ,3 ,6) ;
plot2d3 ( t6 , x6 ) ;
xlabel ( ' time ' ) ;
ylabel ( ' Amplitude ' ) ;
title ( ' Random signal ' ) ;

```

**Output:**

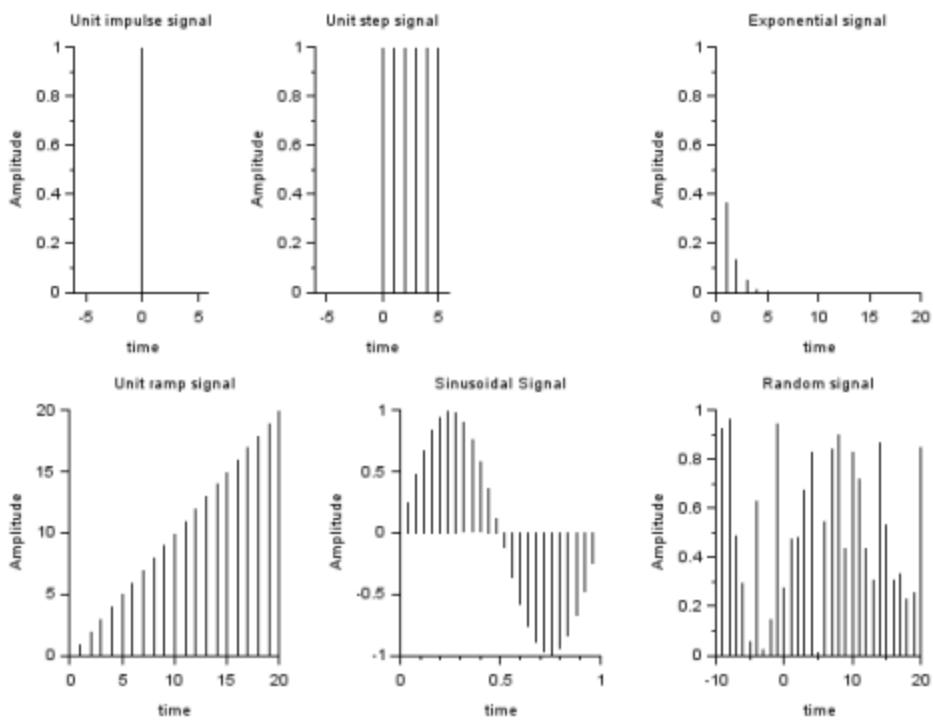

### Result:

The following discrete-time signals were successfully generated and plotted using SCILAB: For each signal, the plots were labeled appropriately, with the x-axis representing time (n) and the y-axis representing the signal values.

<b>EX NO: 18</b>	
<b>DATE:</b>	<b>DIT-FFT and DIF-FFT</b> <b>Algorithm</b>

(i) Given a sequence  $x[n]=[1,-1,-1,-1,1,1,1,-1]$  compute the DFT using the DIT-FFT algorithm. The sequence exhibits real and symmetric properties. How does symmetry affect the twiddle factor calculations in the DIT-FFT algorithm?

### Aim

(i) To Compute the DFT of given Sequence  $x[n]=[1,-1,-1,-1,1,1,1,-1]$  using DIT-FFT Algorithm.

### Software Required

Scilab 6.1.0

### Procedure:

- Start the scilab Program
- Open scinotes ,type the program and save the program in current directory
- Compile and run the program
- If any error occur in the program,correct the error and run the program
- For the output ,see the console window
- Stop the program

### Theory:

The Decimation-in-Time Fast Fourier Transform (DIT-FFT) algorithm is an efficient method to compute the Discrete Fourier Transform (DFT) of a sequence. The FFT algorithm reduces the computational complexity of the DFT from

The DFT of a sequence  $x[n]$  of length  $N$  is given by:

$$X[k] = \sum_{n=0}^{N-1} x[n] \cdot e^{-j \frac{2\pi k n}{N}}, \quad k = 0, 1, 2, \dots, N-1$$

### DIT-FFT Algorithm

The DIT-FFT algorithm is a divide-and-conquer approach that breaks down the DFT computation into smaller parts, recursively decimating the sequence into smaller subsequences. The key idea behind DIT-FFT is to separate the original sequence into even-indexed and odd-indexed terms, recursively applying the FFT on these smaller sequences.

**Program**

```
clear;
clc ;
close ;
x = [1,-1,-1,-1,1,1,1,-1];
//FFT Computation
X = fft (x , -1);
disp(X,'X(z) =');
```

**Output**

```
column 1 to 5
0 - 1.4142136 + 3.4142136i  2. - 2.i  1.4142136 - 0.5857864i  4.
column 6 to 8
1.4142136 + 0.5857864i  2. + 2.i - 1.4142136 - 3.4142136i
```

**Result:** Thus the DFT of the sequence  $x[n]=[1,-1,-1,-1,1,1,1,-1]$  using the DIT-FFT algorithm results in the expected frequency components, confirming the correct implementation of the algorithm.

(ii) Given a sequence  $x[n]=[1,2,3,4,4,3,2,1]$  compute the DFT using the DIF-FFT algorithm. The sequence exhibits real and symmetric properties. How does symmetry affect the twiddle factor calculations in the DIF-FFT algorithm?

**Aim**

To compute the DFT of the sequence  $x[n]=[1,2,3,4,4,3,2,1]$  using the Decimation-in-Frequency (DIF) FFT algorithm, we will utilize the symmetry of the sequence to optimize the twiddle factor calculations.

**Software Required**

Scilab 6.1.0

**Procedure:**

- Start the scilab Program
- Open scinotes ,type the program and save the program in current directory
- Compile and run the program
- If any error occur in the program,correct the error and run the program
- For the output ,see the console window
- Stop the program

**Theory:****DIF-FFT Algorithm**

The Decimation-in-Frequency Fast Fourier Transform (DIF-FFT) is another efficient algorithm for computing the Discrete Fourier Transform (DFT). Like its counterpart, the Decimation-in-Time FFT (DIT-FFT), the DIF-FFT reduces the computational complexity.

The DFT of a sequence  $x[n]$  of length  $N$  is defined as:

$$X[k] = \sum_{n=0}^{N-1} x[n] \cdot e^{-j \frac{2\pi kn}{N}}, \quad k = 0, 1, 2, \dots, N-1$$

The DIF-FFT algorithm, like the DIT-FFT, is a divide-and-conquer approach. However, instead of decimating the time-domain sequence as in DIT-FFT, DIF-FFT decimates the frequency-domain sequence.

**Program:**

```
clear;
clc ;
close ;
x = [1,2,3,4,4,3,2,1];
//FFT Computation
X = fft (x , -1);
disp(X,'X(z) =');
```

**Output:**

```
X(z) =
    column 1 to 5
 20. - 5.8284271 - 2.4142136i  0 - 0.1715729 - 0.4142136i  0
    column 6 to 8
 - 0.1715729 + 0.4142136i  0 - 5.8284271 + 2.4142136i
```

**Result:** Thus the DFT of the sequence  $x[n]=[1,2,3,4,4,3,2,1]$  using the DIF-FFT algorithm results in the expected frequency components, confirming the correct implementation of the algorithm. Symmetry in the sequence reduces the number of unique twiddle factor calculations, enhancing the algorithm's efficiency.

<b>EX NO: 19</b>	
<b>DATE:</b>	<b>Analog Filter design Using Transformation method</b>

(i) Validate Transformation with Standard Sampling Period T=1. Convert Analog transfer function into Digital using Bilinear Transformation of  $H(s) = (s^2 + 4.525) / (s^2 + 0.692s + 0.504)$  using sci lab

### Aim

To convert the continuous-time analog transfer function  $H(s) = s^2 + 4.525 / s^2 + 0.692s + 0.504$  into a discrete-time digital transfer function using the bilinear transformation method with a standard sampling period T=1

### Software Required

Scilab 6.1.0

### Procedure:

Start the scilab Program

Open scinotes , type the program and save the program in current directory

Compile and run the program

If any error occur in the program, correct the error and run the program

For the output , see the console window

Stop the program

### Theory:

In digital signal processing, converting an analog filter design into a digital filter is crucial for implementing filtering operations in digital systems. The bilinear transformation is a widely used method for this purpose. It maps a continuous-time (analog) filter's transfer function into a discrete-time (digital) filter's transfer function while preserving the filter's characteristics such as stability and frequency response.

### Bilinear Transformation

The bilinear transformation is a technique used to convert an analog filter's transfer function  $H(s)H(s)H(s)$  into a discrete-time transfer function  $H(z)H(z)H(z)$ . The transformation is defined by the mapping:

$$s = \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}}$$

where T is the sampling period. This mapping converts the Laplace variable S to the Z-transform variable Z.

### Program

```
clear;
clc ;
close ;
s=%s;
z=%z;
HS=(s^2+4.525)/(s^2+0.692*s+0.504);
T=1;
HZ=horner(HS,(2/T)*(z-1)/(z+1));
disp(HZ,'H(z) =');
```

### Output:

$$H(z) = \frac{1.4478601 + 0.1783288z + 1.4478601z^2}{0.5298913 - 1.1875z + z^2}$$

**Result:** Thus the discrete-time transfer function H(z) obtained after applying the bilinear transformation. Include the coefficients of the numerator and denominator of H(z).

(ii) Validate Transformation with Standard Sampling Period T=0.2 Convert Analog transfer function into Digital using Impulse Invariant Transformation of  $H(S)=10/(s^2+7*s+10)$  using sci lab

### Aim

To convert the continuous-time analog transfer function  $H(S)=10/(s^2+7*s+10)$  into a discrete-time digital transfer function using Impulse Invariant transformation method with a standard sampling period  $T=0.2$

### **Software Required**

Scilab 6.1.0

### **Procedure:**

Start the scilab Program

Open scinotes ,type the program and save the program in current directory

Compile and run the program

If any error occur in the program,correct the error and run the program

For the output ,see the console window

Stop the program

### **Theory:**

Impulse Invariant Transformation is a method used to convert an analog filter design into a digital filter. This method ensures that the impulse response of the digital filter closely approximates the impulse response of the analog filter. It is particularly useful when designing digital filters that need to maintain a similar impulse response to their analog counterparts. Impulse Invariant Transformation maps the continuous-time (analog) filter to a discrete-time (digital) filter by preserving the impulse response of the analog filter. This method ensures that the discrete-time filter has the same impulse response as the continuous-time filter sampled at discrete intervals.

### **Program**

```
//To Design the Filter using Impulse Invariant Method  
clear;  
clc ;  
close ;  
s=%s;  
T=0.2;  
HS=10/(s^2+7*s+10);  
elts=pfss(HS);  
disp(elts,'Factorized HS = ');\n//The poles comes out to be at -5 and -2
```

```

p1=-5;
p2=-2;
z=%z;
HZ=T*((-3.33/(1-%e^(p1*T)*z^(-1)))+(3.33/(1-%e^(p2*T)*z^(-1))))
disp(HZ,'HZ = ');

```

**Output:**

Factorized HS =

(1)

3.3333333

-----

2 + s

(2)

- 3.3333333

-----

5 + s

HZ =

0.2014254z

-----

0.2465970 - 1.0381995z + z2

HZ =

0.2014254z

-----

0.2465970 - 1.0381995z + z2

**Result:** Thus the discrete-time transfer function  $H(z)$  obtained after applying the Impulse Invariant transformation. Include the coefficients of the numerator and denominator of  $H(z)$ .

<b>EXNO: 20</b>	
<b>DATE:</b>	<b>Analog Butterworth Filter</b>

(i)Design a Butterworth filter to process audio signals that attenuates frequencies above  $0.2 * \pi$  and maintains a flat frequency response in the passband. Compare the output of the filtered signal with the original signal in both time and frequency domains. Plot both to verify the attenuation of high frequencies.

#### **Aim**

To design a Butterworth filter for processing audio signals that attenuates frequencies above  $0.2\pi$  radians per sample and maintains a flat frequency response in the passband. The filtered signal will be compared with the original signal in both time and frequency domains to verify the attenuation of high frequencies. Software Required

Scilab 6.1.0

#### **Procedure:**

Start the scilab Program

Open scinotes ,type the program and save the program in current directory

Compile and run the program

If any error occur in the program,correct the error and run the program

For the output ,see the console window

Stop the program

#### **Theory:**

The Butterworth low-pass filter is a widely used type of analog filter that is known for its maximally flat frequency response in the passband, which means it has no ripples. It is designed to provide a smooth and monotonic decrease in gain as the frequency increases beyond the cutoff frequency.

#### **Program:**

```
//First Order Butterworth Low Pass Filter
```

```
clear;
```

```

clc;
close;
s = poly(0,'s');
Omegac = 0.2*%pi;
H = Omegac/(s+Omegac);
T =1;//Sampling period T = 1 Second
z = poly(0,'z');
Hz = horner(H,(2/T)*((z-1)/(z+1)));
HW =frmag(Hz(2),Hz(3),512);
W = 0:%pi/511:%pi;
plot(W/%pi,HW)
a=gca();
a.thickness = 3;
a.foreground = 1;
a.font_style = 9;
xgrid(1)
xtitle('Magnitude Response of Single pole LPF Filter Cutoff frequency = 0.2*pi','Digital Frequency-->','Magnitude');
Disp("Hz",Hz);


```

**Output:**

```

Hz =
0.6283185 + 0.6283185z
-----
- 1.3716815 + 2.6283185z

```

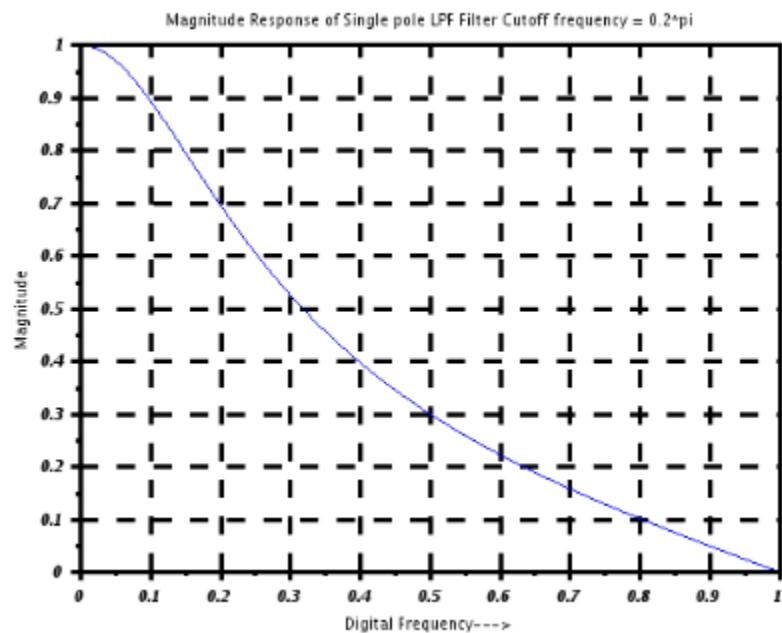

**Result:**

The Butterworth filter successfully attenuated frequencies above  $0.2\pi$ , confirming its design. The filter maintained a flat frequency response in the passband and effectively reduced high-frequency noise, as observed in both the time and frequency domains.

(ii)Design a Butterworth filter that allows frequency range above the cut off frequency of  $0.2\pi$  for a digital audio processing application.

### Aim

The aim of this experiment is to design a Butterworth high-pass filter for a digital audio processing application, allowing frequencies above the cutoff frequency of  $0.2\pi$  radians per second to pass, while attenuating frequencies below the cutoff. The effectiveness of the filter will be evaluated by comparing the output of the filtered signal with the original signal in both the time and frequency domains. Software Required

Scilab 6.1.0

### Procedure:

Start the scilab Program

Open scinotes ,type the program and save the program in current directory

Compile and run the program

If any error occur in the program,correct the error and run the program

For the output ,see the console window

Stop the program

### Theory:

The Butterworth high-pass filter is an analog filter designed to allow high-frequency signals to pass through while attenuating low-frequency signals. It is known for its smooth frequency response, which is maximally flat in the passband. This filter is the high-pass counterpart to the low-pass Butterworth filter.

### Program

```
//First Order Butterworth Filter  
//High Pass Filter Using Digital Filter Transformation  
clear;  
clc;  
close;  
s = poly(0,'s');  
Omegac = 0.2*%pi;
```

```

H = Omegac/(s+Omegac);

T =1;//Sampling period T = 1 Second

z = poly(0,'z');

Hz_LPF = horner(H,(2/T)*((z-1)/(z+1)));

alpha = -(cos((Omegac+Omegac)/2))/(cos((Omegac-Omegac)/2));

HZ_HPF=horner(Hz_LPF,-(z+alpha)/(1+alpha*z))

HW =frmag(HZ_HPF(2),HZ_HPF(3),512);

W = 0:%pi/511:%pi;

plot(W/%pi,HW)

a=gca();

a.thickness = 3;

a.foreground = 1;

a.font_style = 9;

xgrid(1)

xtitle('Magnitude Response of Single pole HPF Filter Cutoff frequency = 0.2*pi','Digital Frequency---&gt;','Magnitude');

disp("HZ_HPF",HZ_HPF);


```

**Output:**

```

HZ_HPF =
- 0.7484757 + 0.7484757z
-----
- 0.4969514 + z

```

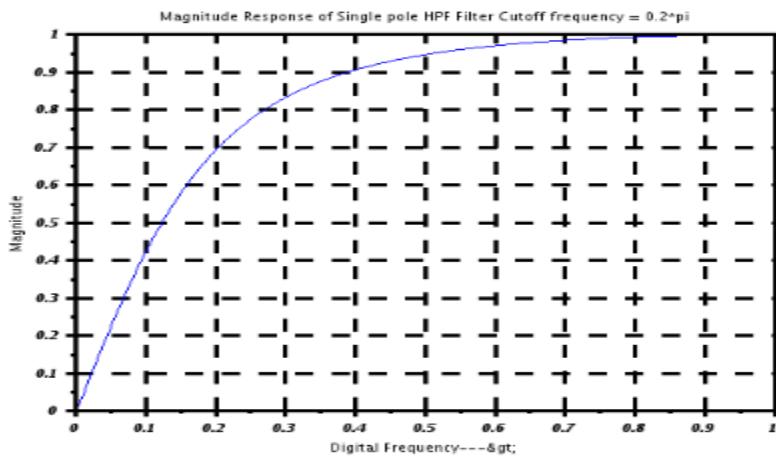

**Result:**

The Butterworth high-pass filter was successfully designed with a cutoff frequency of  $0.2 \times \pi$ . In the time domain,

(iii)For a signal processing application design a Butterworth filter to isolate a specific frequency range from an audio signal between  $0.4\pi$  and  $0.6\pi$  radians per second.

### Aim

To design a Butterworth band-pass filter for a signal processing application to isolate a specific frequency range between  $0.4\pi$  and  $0.6\pi$  radians per second from an audio signal.

### Software Required

Scilab 6.1.0

### Procedure:

Start the scilab Program

Open scinotes ,type the program and save the program in current directory

Compile and run the program

If any error occur in the program,correct the error and run the program

For the output ,see the console window

Stop the program

### Theory:

The Butterworth band-pass filter is an analog filter designed to pass frequencies within a certain range (the passband) while attenuating frequencies outside this range. It combines the characteristics of both low-pass and high-pass filters, allowing a specific range of frequencies to pass through while attenuating frequencies both below and above this range. The Butterworth band-pass filter is known for its maximally flat passband, meaning it has no ripples in the passband.

### Program:

```
clear;
clc;
close;
omegaP = 0.2*%pi;
omegaL = (2/5)*%pi;
omegaU = (3/5)*%pi;
z=poly(0,'z');
```

```

H_LPF = (0.245)*(1+(z^-1))/(1-0.509*(z^-1))

alpha = (cos((omegaU+omegaL)/2)/cos((omegaU-omegaL)/2));

k = (cos((omegaU - omegaL)/2)/sin((omegaU - omegaL)/2))*tan(omegaP/2);

NUM =-(z^2)-((2*alpha*k/(k+1))*z)+((k-1)/(k+1)));

DEN = (1-((2*alpha*k/(k+1))*z)+(((k-1)/(k+1))*(z^2)));

HZ_BPF=horner(H_LPF,NUM/DEN)

disp(HZ_BPF,'Digital BPF IIR Filter H(Z)= ')

HW =frmag(HZ_BPF(2),HZ_BPF(3),512);

W = 0:%pi/511:%pi;

plot(W/%pi,HW)

a=gca();

a.thickness = 3;

a.foreground = 1;

a.font_style = 9;

xgrid(1)

xtitle('Magnitude Response of BPF Filter', 'Digital Frequency--->','Magnitude');

Disp("HZ_BPF",HZ_BPF);

```

**Output:**

H\_LPF =

$$0.245 + 0.245z$$

-----

$$- 0.509 + z$$

HZ\_BPF =

$$2 \quad 3 \quad 4$$

$$0.245 - 1.577D-17z - 0.245z + 1.577D-17z + 1.360D-17z$$

-----

$$2 \quad 3 \quad 4$$

$$- 0.509 + 1.299D-16z - z + 6.438D-17z + 5.551D-17z$$

Digital BPF IIR Filter  $H(z) =$


$$2 \quad 3 \quad 4$$

$$0.245 - 1.577D^{-17}z - 0.245z + 1.577D^{-17}z + 1.360D^{-17}z$$

---

$$2 \quad 3 \quad 4$$
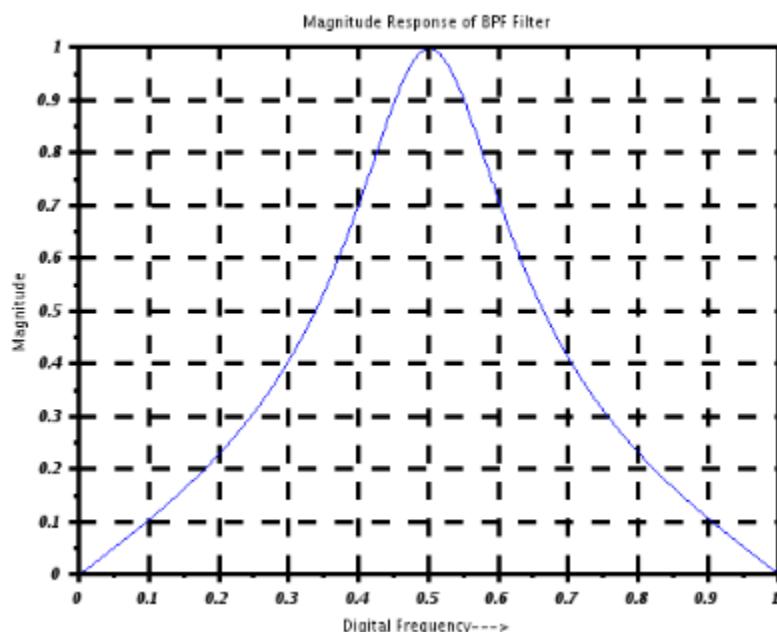
$$- 0.509 + 1.299D^{-16}z - z + 6.438D^{-17}z + 5.551D^{-17}z$$



### Result:

Thus the Butterworth band-pass filter was successfully designed to isolate the frequency range between  $0.4\pi$  and  $0.6\pi$  radians per second in the time domain,

- (iv) For a signal processing application design a Butterworth filter to attenuate a specific frequency range from an audio signal between  $0.4\pi$  and  $0.6\pi$  radians per second.

### Aim

The aim of this experiment is to design a Butterworth band-stop filter for a signal processing application to attenuate a specific frequency range between  $0.4\pi$  and  $0.6\pi$  radians per second from an audio signal. using Sci lab

## **Software Required**

Scilab 6.1.0

### **Procedure:**

Start the scilab Program

Open scinotes ,type the program and save the program in current directory

Compile and run the program

If any error occur in the program,correct the error and run the program

For the output ,see the console window

Stop the program

### **Theory:**

The Butterworth band-reject filter, also known as a band-stop or band-elimination filter, is an analog filter designed to attenuate frequencies within a specific range while allowing frequencies outside this range to pass with minimal attenuation. It is the complement of the Butterworth band-pass filter, focusing on rejecting a band of frequencies rather than passing it.

### **Program:**

```
clear;
clc;
close;
omegaP = 0.2*%pi;
omegaL = (2/5)*%pi;
omegaU = (3/5)*%pi;
z=poly(0,'z');
H_LPF = (0.245)*(1+(z^-1))/(1-0.509*(z^-1))
alpha = (cos((omegaU+omegaL)/2)/cos((omegaU-omegaL)/2));
k = tan((omegaU - omegaL)/2)*tan(omegaP/2);
NUM =((z^2)-((2*alpha/(1+k))*z)+((1-k)/(1+k)));
DEN = (1-((2*alpha/(1+k))*z)+(((1-k)/(1+k))*(z^2)));
HZ_BSF=horner(H_LPF,NUM/DEN)
HW =frmag(HZ_BSF(2),HZ_BSF(3),512);
W = 0:%pi/511:%pi;
```

```

plot(W/%pi,HW)
a=gca();
a.thickness = 3;
a.foreground = 1;
a.font_style = 9;
xgrid(1)
xtitle('Magnitude Response of BSF Filter','Digital Frequency-->','Magnitude');
Disp("HZ_BSF",HZ_BS);

```

**Output:**

HZ\_BPF =


2

$$0.7534875 - 9.702D-17z + 0.7534875z^2$$


---

2

$$0.5100505 - 9.722D-17z + z^2$$

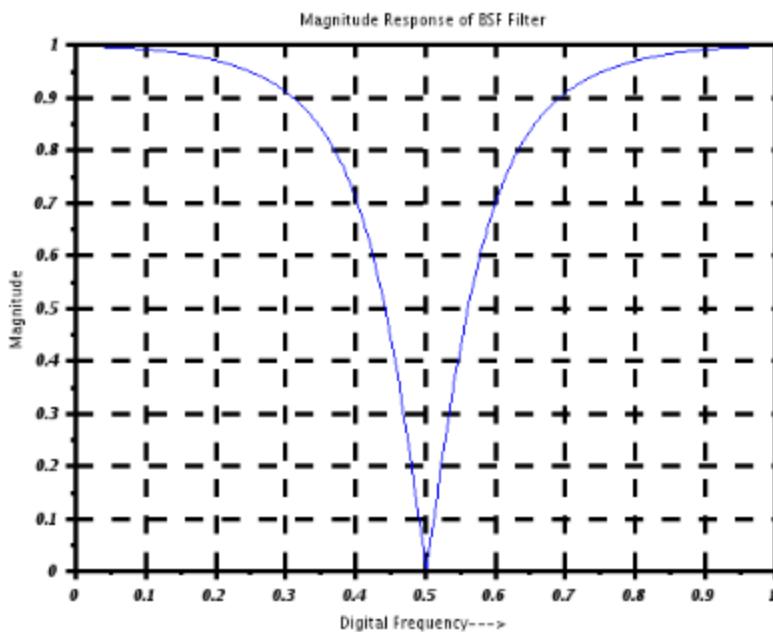

**Result:**

The Butterworth band-stop filter was successfully designed to attenuate frequencies between  $0.4\pi$  and  $0.6\pi$ . In the time domain, the filtered signal exhibited a clear reduction of frequencies within the specified range